

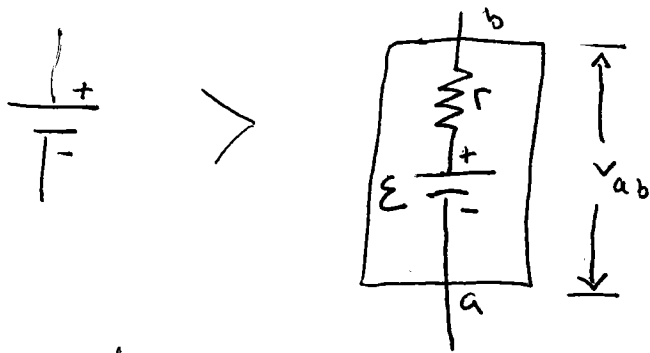


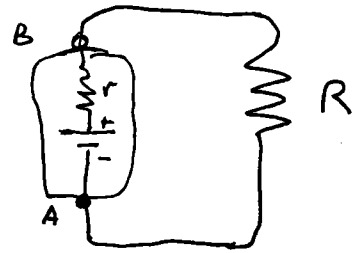All batteries + Motors have a little internal resistance



$$V_{ab} = \epsilon - ir$$


(Volts Potential)

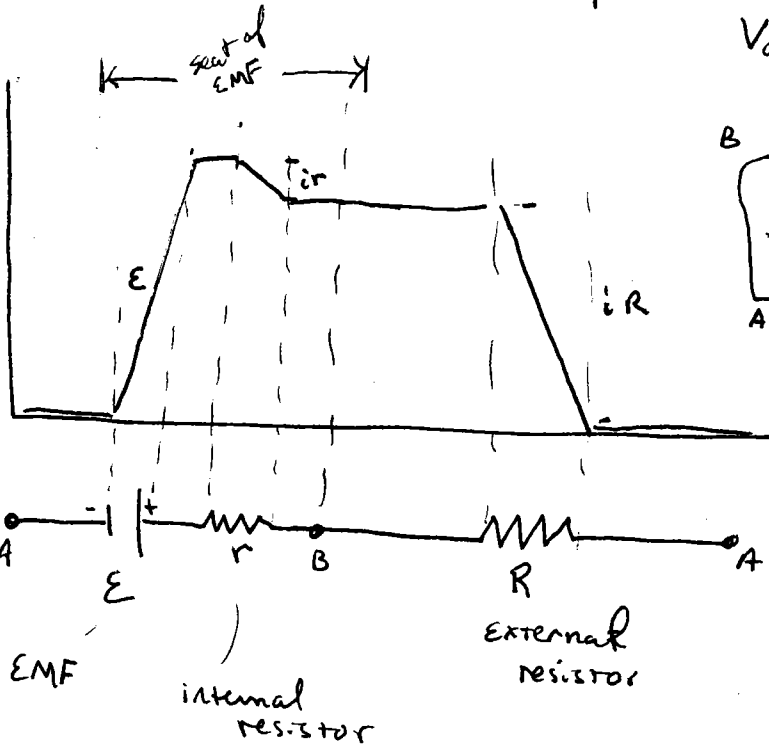

Kirchoff's Rules Apply to circuits:

- 1) When any closed-circuit loop is traversed, the Algebraic  $\sum$  of the changes in potential is zero.
- 2) At any junction point where the current can divide current is conserved, i.e.  $\sum \text{current in} = \sum \text{current out}$

e.g.

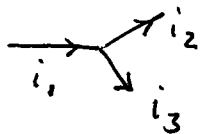


$$i_1 = i_2 + i_3$$


$\sum V$  across closed loop in circuit = 0

$\therefore V - iR = 0$

$V = iR$

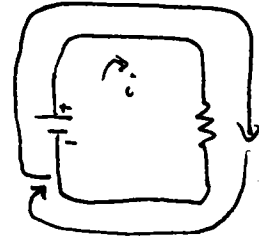

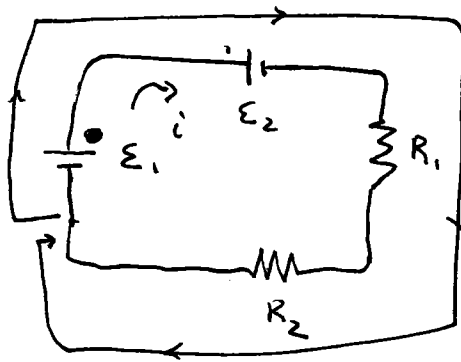if EMF traversed in direction of EMF during  $\sum$  sign is +  
 " " " against " " " " -  
 if resistor traversed in direction of current  
 The sign of change in potential is -  
 otherwise it is +




~ Part of  $\mathcal{E}$

$\mathcal{E}_1 - \mathcal{E}_2 - iR_1 - iR_2 = 0$

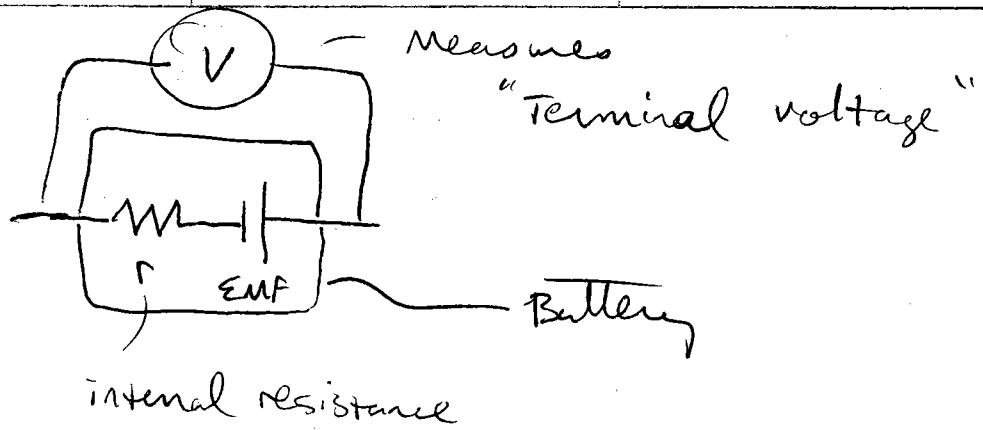14-782 500 SHEETS FILLER 5 SQUARE  
 42-361 50 SHEETS EYE-EASER 5 SQUARE  
 42-362 100 SHEETS EYE-EASER 5 SQUARE  
 42-363 200 SHEETS EYE-EASER 5 SQUARE  
 42-364 100 SHEETS EYE-EASER 5 SQUARE  
 42-365 100 RECYCLED WHITE 5 SQUARE  
 42-366 200 RECYCLED WHITE 5 SQUARE  
 Made in U.S.A.






Voltmeter measures drop in potential across two points


Always connected in Parallel!

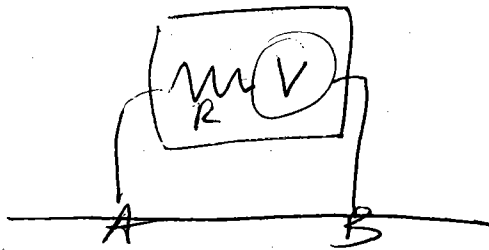Large  $R$  keeps current flow negligible




Ammeter measures current through a segment of wire.

Always connected in Series

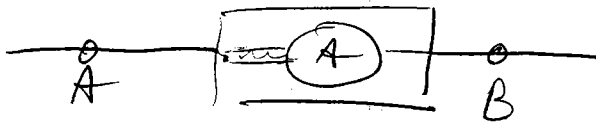

All current goes thru it  
(low resistance)

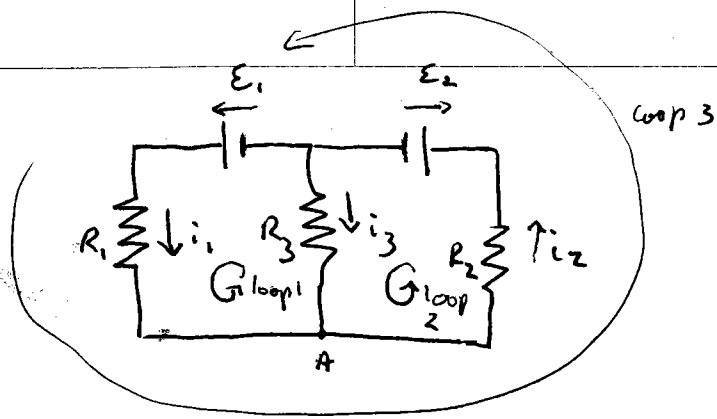Can burn up voltmeter if you hook it up in series.



Know values of  $E_1, E_2, R_1, R_2, R_3$   
 Find  $i_1, i_2, i_3$

NOTES:

→ Sometimes (like above) problem ignores internal resistance of battery  
 Flow with it ... but be on lookout for it

→ Choose directions for currents. It does NOT matter that  
 you don't know actual directions (if you get it wrong  
 at the start  $i$  will come out negative)

loop 1:

$$E_1 - i_1 R_1 + i_3 R_3 = 0$$

I eqn

loop 2:

$$-E_2 - i_3 R_3 - i_2 R_2 = 0$$

II eqn

loop 3:

$$E_1 - i_1 R_1 - i_2 R_2 - E_2 = 0$$

NOT independent  
 just sum of 1st two eqns

at pt A

$$i_1 + i_3 - i_2 = 0$$

III eqn

3 equations, 3 unknowns can solve for  $i_1, i_2, i_3$

[if one of the  $i$ 's comes out negative then it tells you that  
 your initial choice of direction for that  $i$  was incorrect]

With just  $i$ 's and  $R$ 's will get steady currents  
 and voltages

500 SHEETS, FILLER 5 SQUARE  
 100 SHEETS, FILLER 5 SQUARE  
 100 SHEETS, FILLER 5 SQUARE  
 100 SHEETS, FILLER 5 SQUARE  
 200 SHEETS, FILLER 5 SQUARE  
 100 RECYCLED WHITE 5 SQUARE  
 42-389 200 RECYCLED WHITE 5 SQUARE  
 42-389 200 RECYCLED WHITE 5 SQUARE  
 5200 m U S A

