
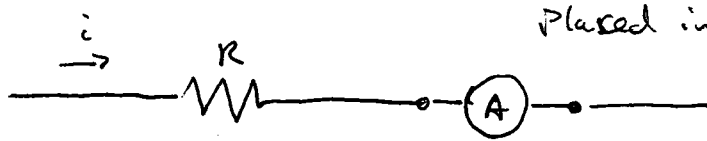


Measure currents w/ Ammeter

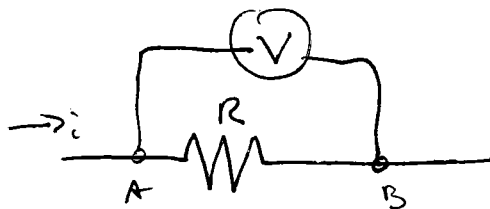


Placed in series at pt where you want to measure current

Measure Voltage drops w/ voltmeter



Placed in parallel across the two pts where you want to measure ΔV

RC Circuits

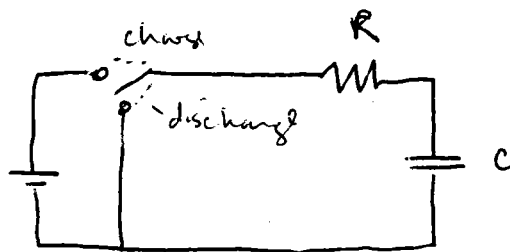

When switch in charging position

$$\sum V = 0 \quad \varepsilon - iR - q/C = 0$$

\uparrow \uparrow
 V_R V_C




q is a function of Time

Differential Equation

$$\varepsilon = \frac{dq}{dt} R + q/C$$



\hookrightarrow has soln $q = C\varepsilon(1 - e^{-t/RC})$

Substitute in and work out

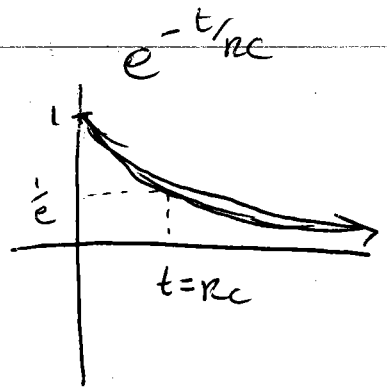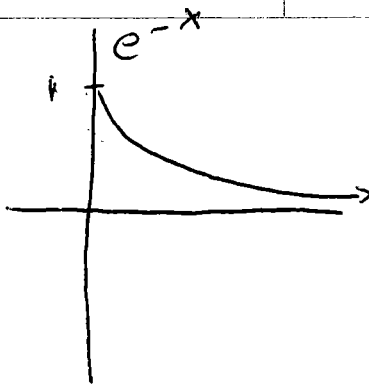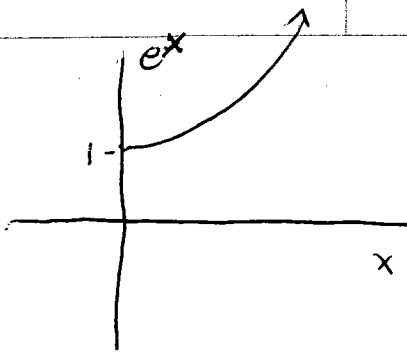

$$1 - e^{-t/RC}$$

$$q = CE(1 - e^{-t/RC})$$

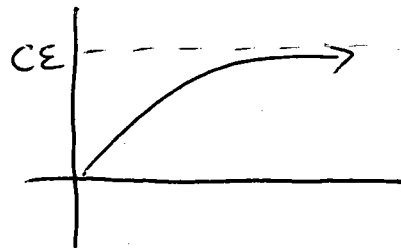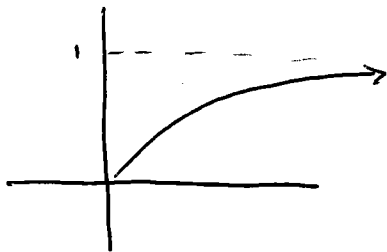


$$CV = q$$

$RC \equiv$ time constant

IF RC large, takes a long time to charge up capacitor
 " " small, " short " "

$T = RC =$ time it takes to charge up to within $\frac{1}{e}$ of final value

Now discharge

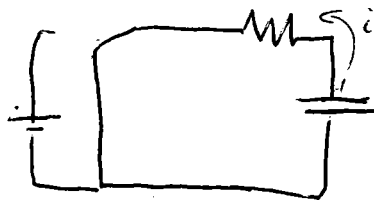

$$\frac{q}{C} - iR = 0$$

$$i = -\frac{dq}{dt}$$

$$\frac{q}{C} + \frac{dq}{dt} R = 0$$


$$\frac{q}{C} = -\frac{dq}{dt} R$$

$$\int_0^t \frac{dt}{RC} = \int_{q_0}^q \frac{dq}{q}$$

$$-\frac{t}{RC} = \ln \frac{q}{q_0}$$

$$e^{-t/RC} = q/q_0$$

$$q = q_0 e^{-t/RC}$$

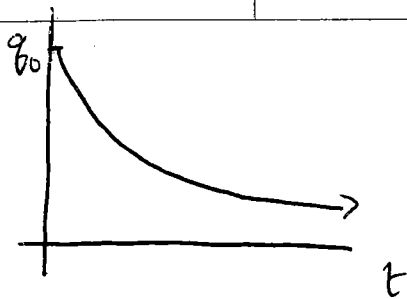

again RC dictates how fast
charge drains off

know $q(t)$ can calculate $i(t)$

$V(t)$ across resistor

$V(t)$ across capacitor

Stored Energy (t) in capacitor

etc.

⋮

Magnetism - Magnetostatics

Put in a good Magnetic field Demo!

There exists a Magnetic field - can affect charged particles

$$\vec{F} = q \vec{v} \times \vec{B}$$

B units 1 Tesla = $1 \frac{N}{A \cdot m}$ SI

common unit of cgs system = gauss CGS

$$1 \text{ Gauss} = 10^{-4} \text{ Tesla}$$