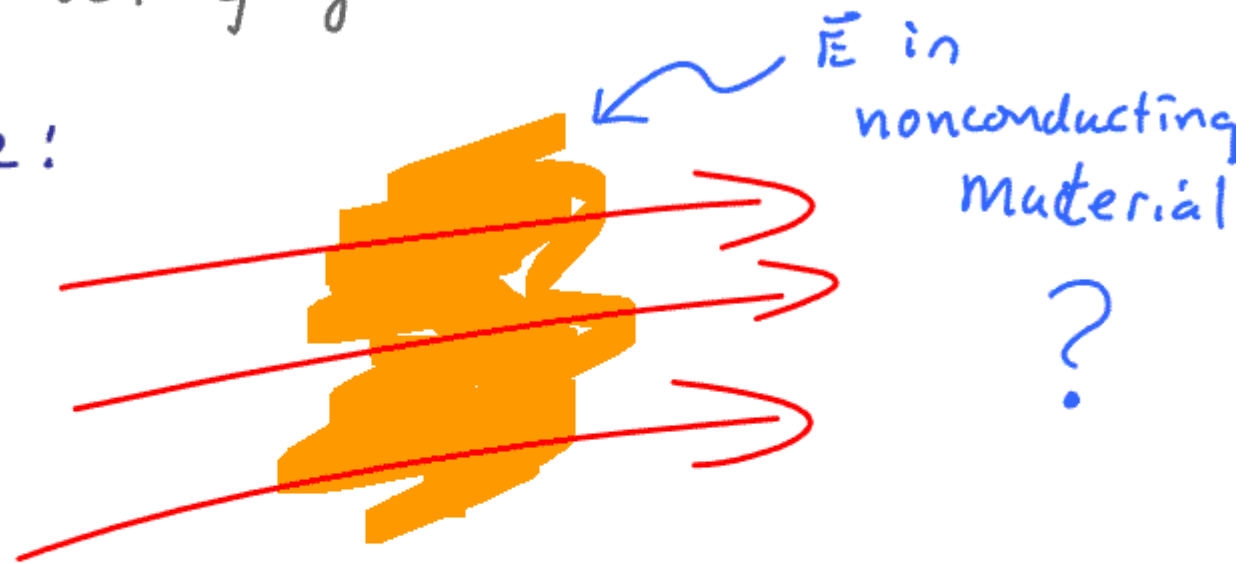


Physics 114 - March 2, 2006

Trouble-shooting guide


Last time!



$$E = \frac{E_0}{\{K\}} \quad \text{--- dielectric constant}$$

or can use $\epsilon \equiv$ Permittivity
rather than ϵ_0 $\epsilon \equiv K\epsilon_0$

K, ϵ are Material dependent

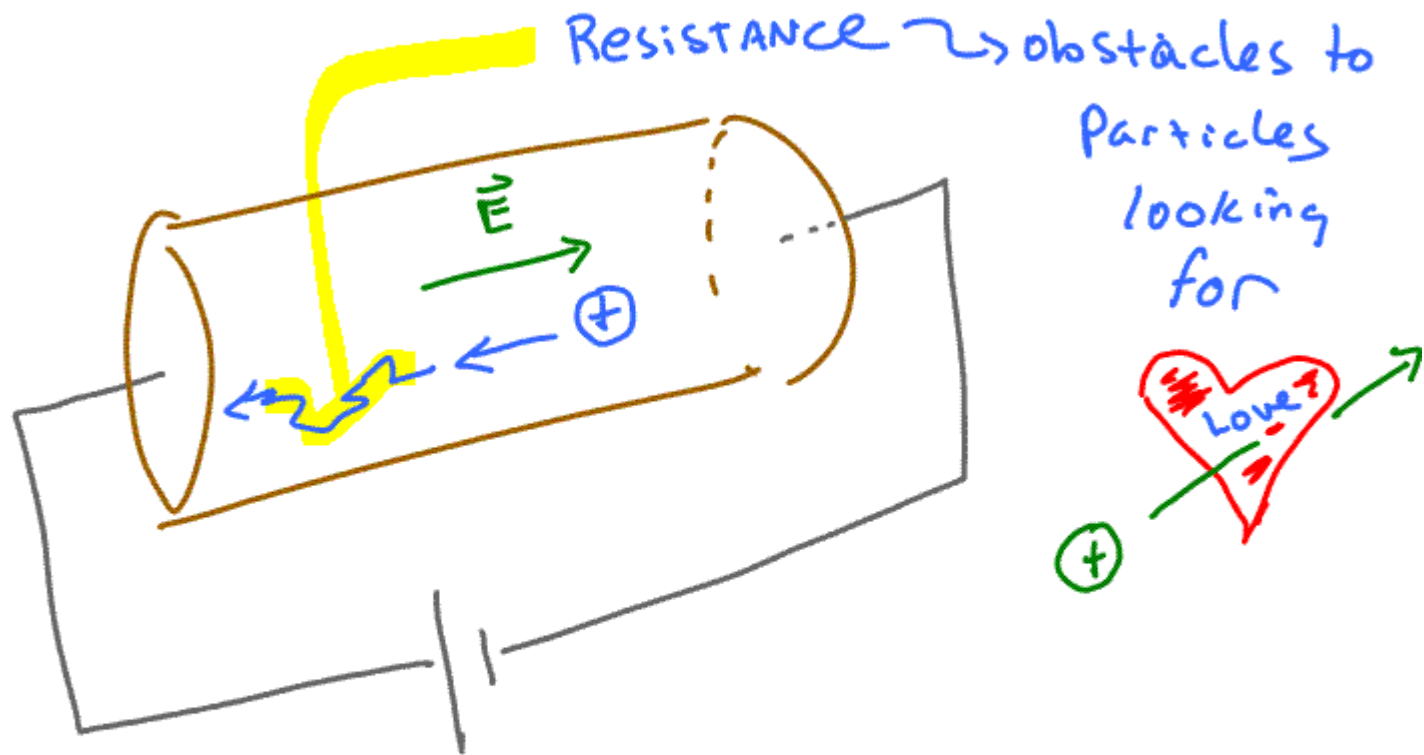

Charges flow $i = \frac{dq}{dt}$ in Amperes

$$1 \text{ Ampere} = \frac{1 \text{ coul}}{1 \text{ second}}$$



André Marie Ampère
(1775 - 1836)

French { mathematician
chemist
physicist

The inspiration for
Elvis' Collar

$$V = IR$$

Ohm's Law



Georg
Ohm

RESISTANCE
measured
in
Ohms

$$1 \text{ Ohm} = 1 \frac{\text{volt}}{\text{Ampere}}$$

Ω

1789-1854

German

Power spent in resistor

→ heat

$$i = \frac{v}{R}$$

lacks R

$$P = i v$$

$$v = i R$$


$$P = i^2 R$$

lacks v

$$P = \frac{v^2}{R}$$

lacks i

use the one that works

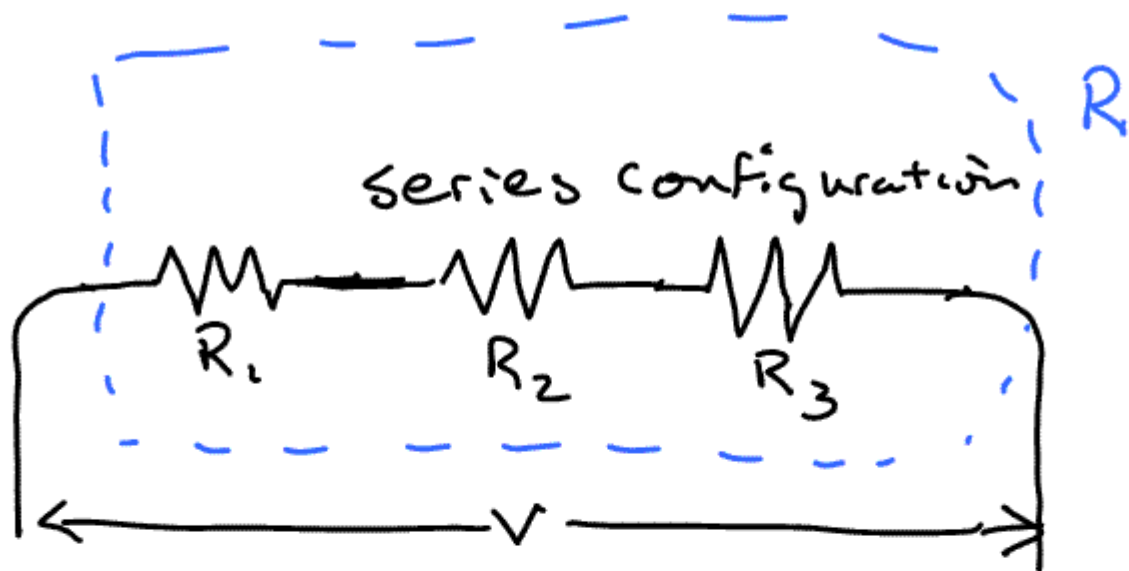


$$V = V_1 + V_2 + V_3 = iR_1 + iR_2 + iR_3 = i(R_1 + R_2 + R_3)$$
$$= iR$$

$$R = R_1 + R_2 + R_3 = \sum_i R_i$$

Resistors in Series

$$R = \sum_i R_i$$

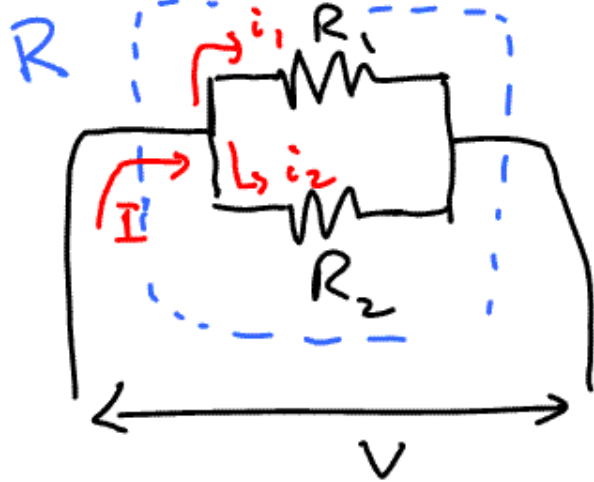

Resistors
in
Parallel

$$V = IR$$

$$V = i_1 R_1$$

$$V = i_2 R_2$$


$$I = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$


ΔV relative to PTA

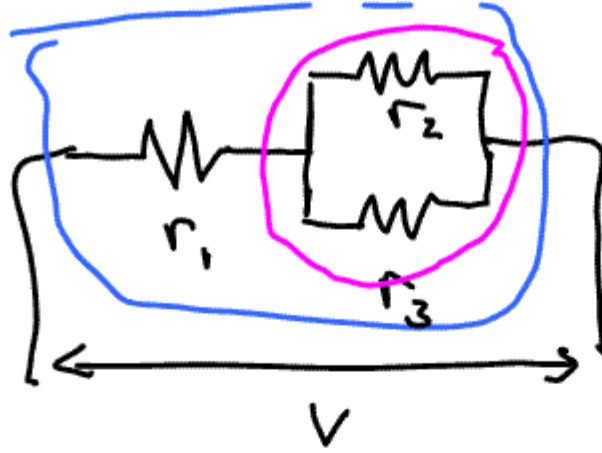

$V = \epsilon$

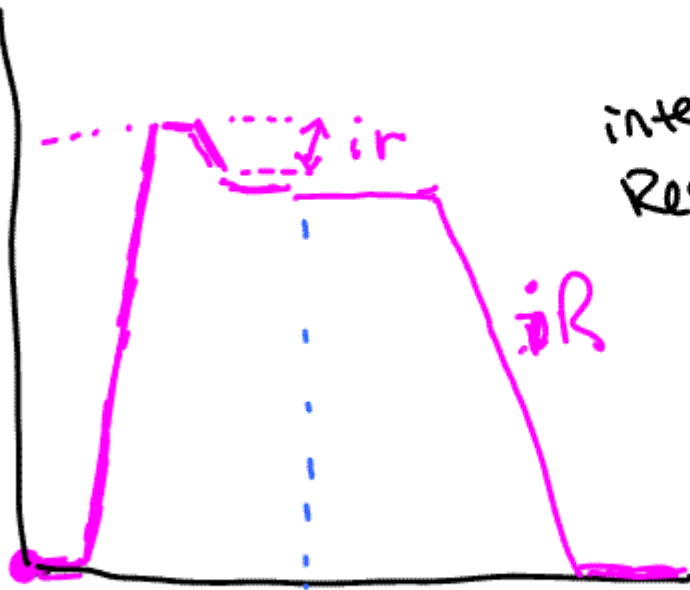


internal Resistance

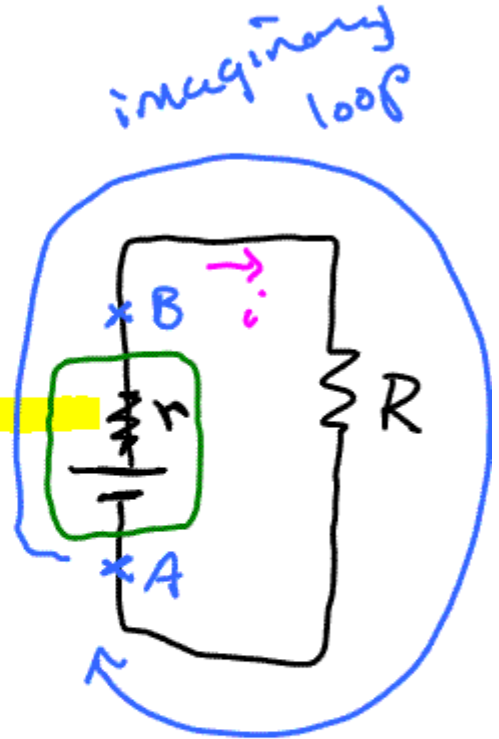

$V_A = 0$


loop distance

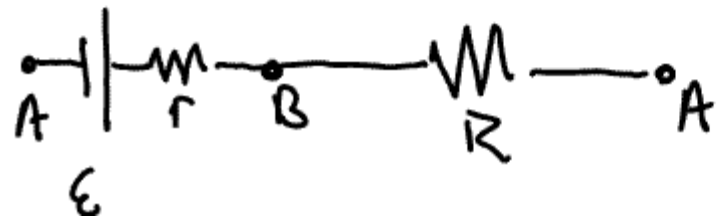

Battery \rightarrow V CONSTANT
one direction


Direct Current

DC

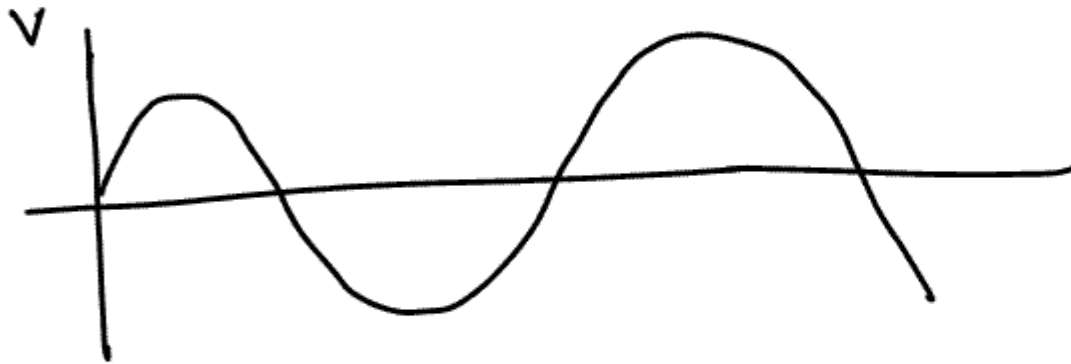

Alternating
current

AC

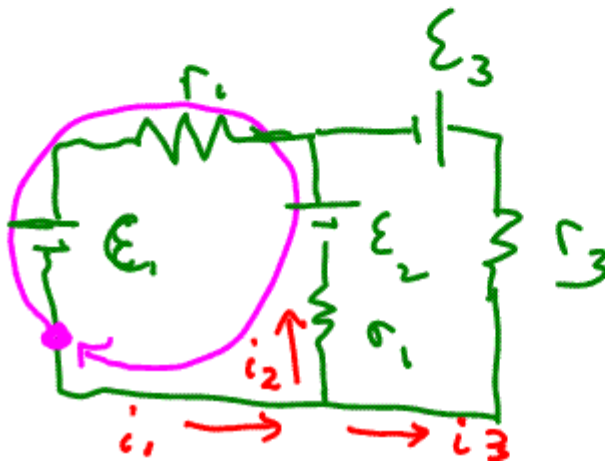

$$i_1 = i_2 + i_3$$

Kirchoff's Rules:

① $\sum V = 0$ around closed loop in circuit

② $\sum i = 0$ at any junction

Current is conserved at
any branch point

use rules and independent loops
and conventions

To get N eqns




↳ solve for N
unknowns



Solve a problem \rightarrow conventions

Choose currents in each branch of circuit
(arbitrary)

Imaginary loops about circuit

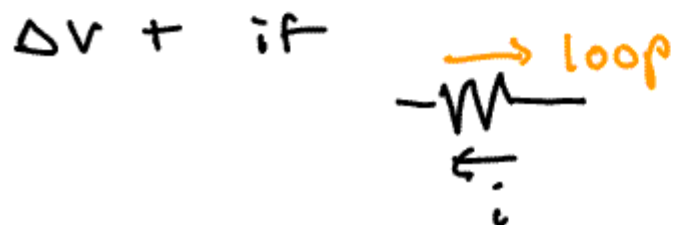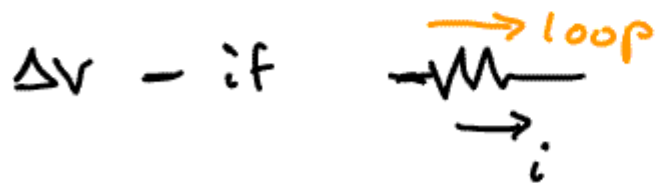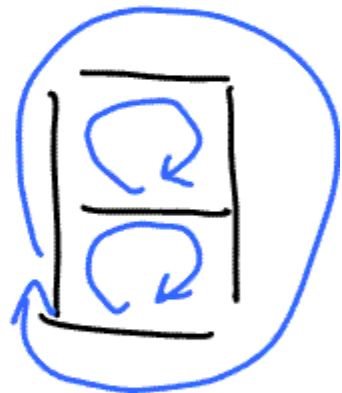Sum ΔV as go around
each independent
imaginary loop



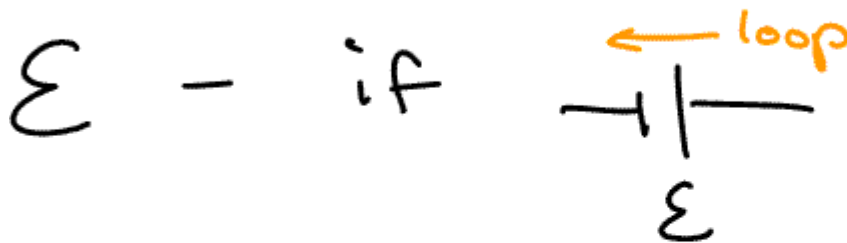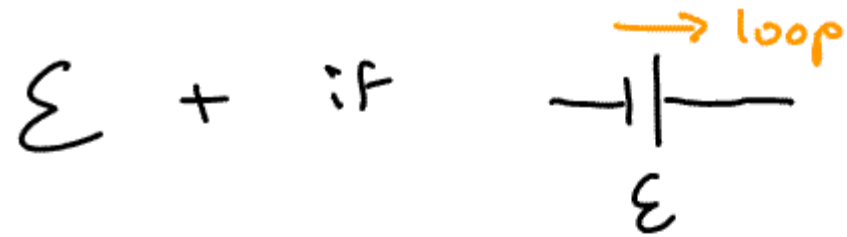


Each indep loop

$\rightarrow N$ eqns

Solve N unk

$$\Sigma V = 0$$

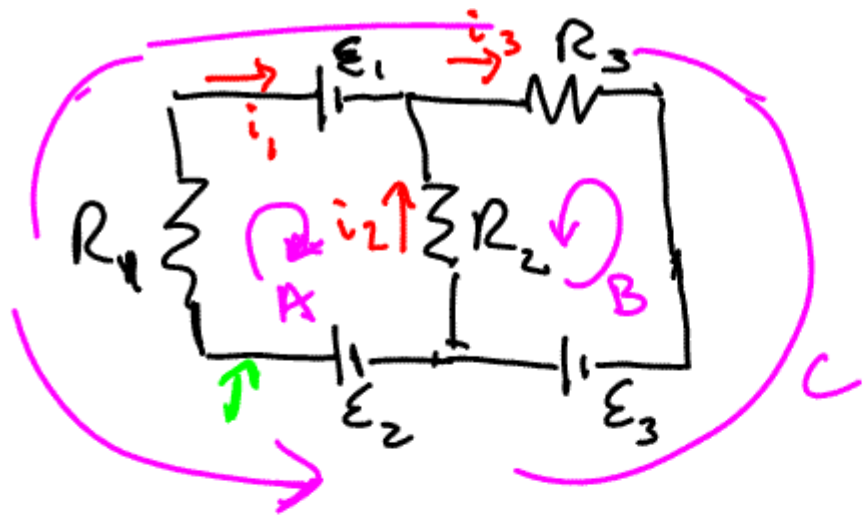

$$i_1 + i_2 = i_3$$

$\sum V = 0$ around each loop

A $\sum V = -i_1 R_1 - \epsilon_1 + i_2 R_2 + \epsilon_2 = 0$

B $\sum V = -\epsilon_3 + i_3 R_3 + i_2 R_2 = 0$

gives 3 eqns \rightarrow can solve for up to 3 unknowns