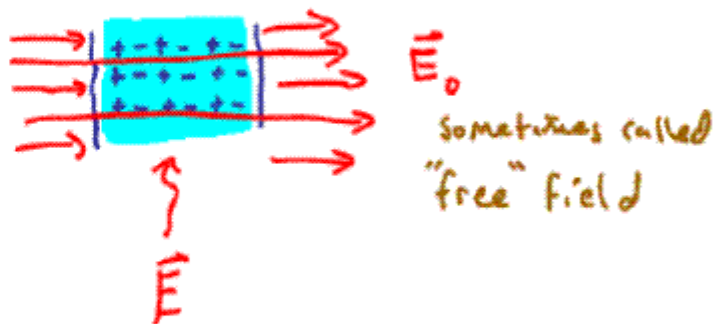


Physics 142 - October 11, 2007

EXAM 1 - soon ...

Last Time -

- Dielectrics



$$\vec{E} = \frac{\vec{E}_0}{\kappa}$$

$\kappa \equiv$ dielectric constant > 1

$$\frac{1}{\kappa} = \epsilon \equiv \text{permittivity}$$

- current

$$I \text{ or } i = \frac{dq}{dt}$$

$+i$ is direction of + charge flow

- Resistance

$$V = IR$$

Ohm's Law

RESISTANCE

unit
ohm $\equiv \Omega$

Impedes electrons "Looking" for love 

Pass current thru resistor - Energy lost as heat or light

Power dissipated $\equiv P = iV = i^2R = i^2R$ Mostly

~~$P = i^2R$~~

$$V = iR$$

$$i = V/R$$

$$P = \frac{V^2}{R}$$

Possible Source of Confusion

Resistors:

Capacitors:

Series




$$R = \sum_i R_i$$

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

Parallel

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

$$C = \sum_i C_i$$

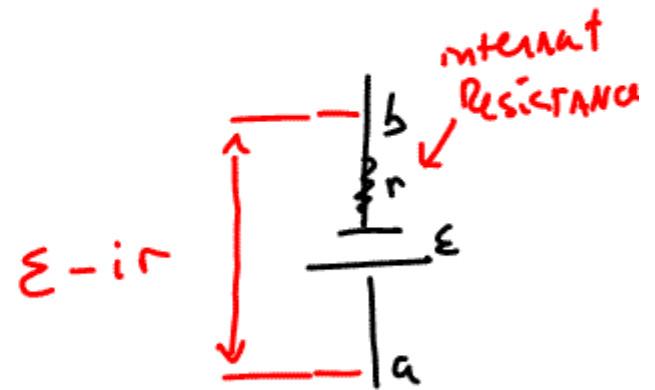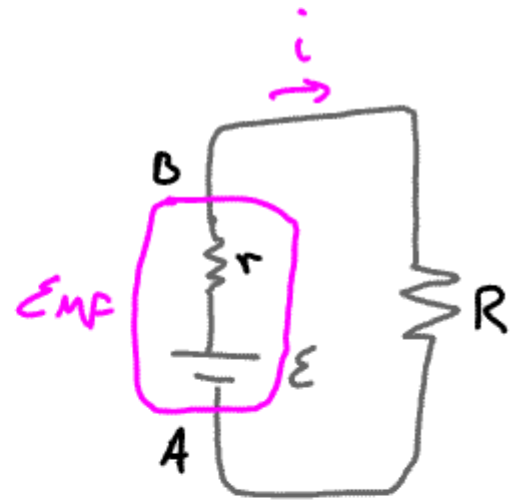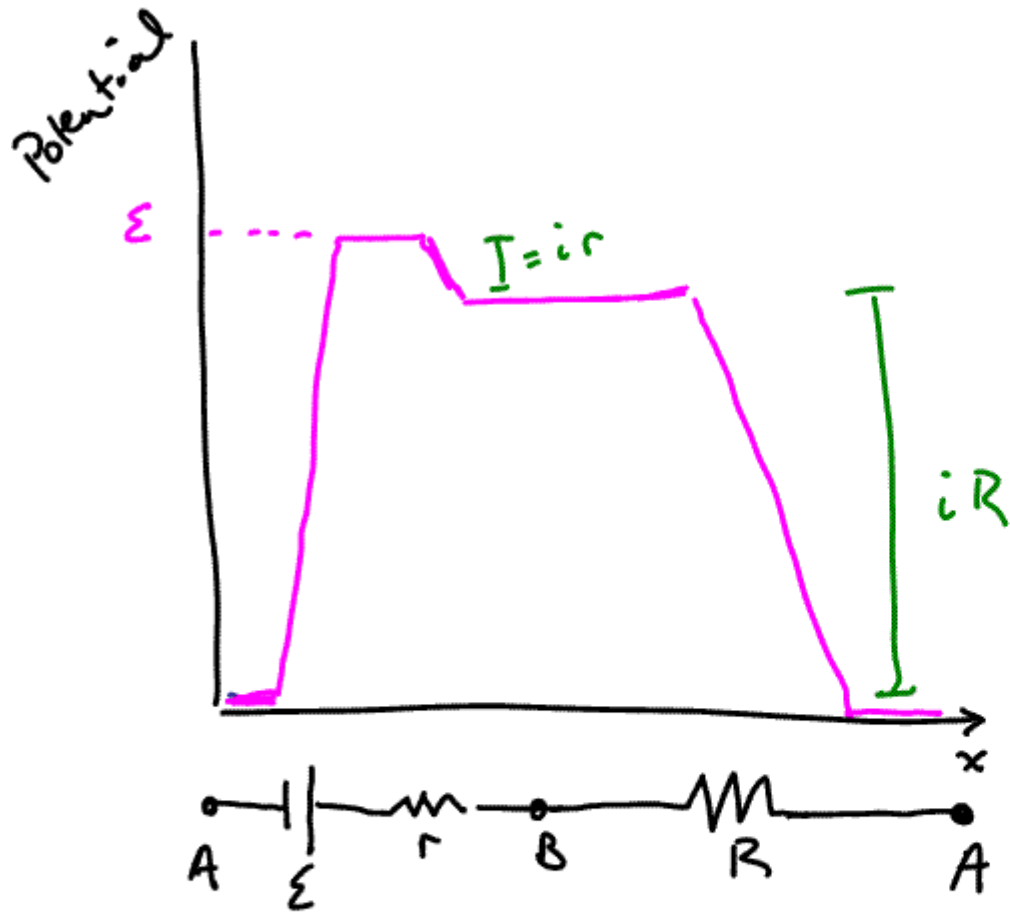

$$V_A = 0$$

Assuming DC
direct current


for now

Kirchoff's rules

know $\mathcal{E}_1, \mathcal{E}_2$

R_1, R_2, R_3

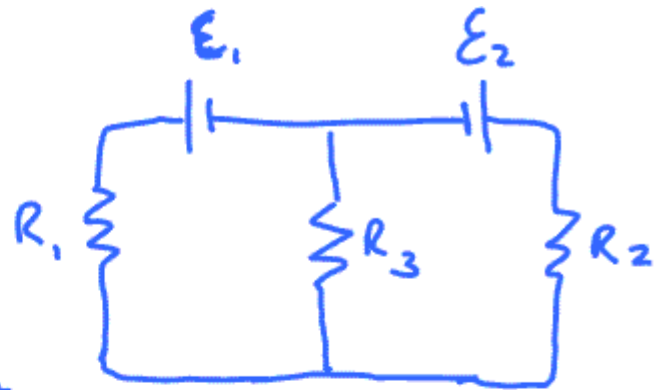want currents throughout
circuit \rightarrow how?



Kirchoff's Rules:

- ① $\sum V = 0$ around closed loop in circuit
- ② current is conserved at any
BRANCH point in circuit

use these rules to create N independent equations
to solve for N unknowns


Convention [told this is opposite that of ECE 210]
↳ no matter if consistent

choose currents in each branch (arbitrary)

Sum ΔV across each circuit component as you go around an imaginary closed loop in the circuit

$\Delta V - iR$ if 

$\mathcal{E} +$ if 


$\Delta V + iR$ if 

$\mathcal{E} -$ if 

Get N eqns, N unknowns and solve

Tedious \rightarrow must be careful and consistent
w/ Conventions and Signs

use only independent loops

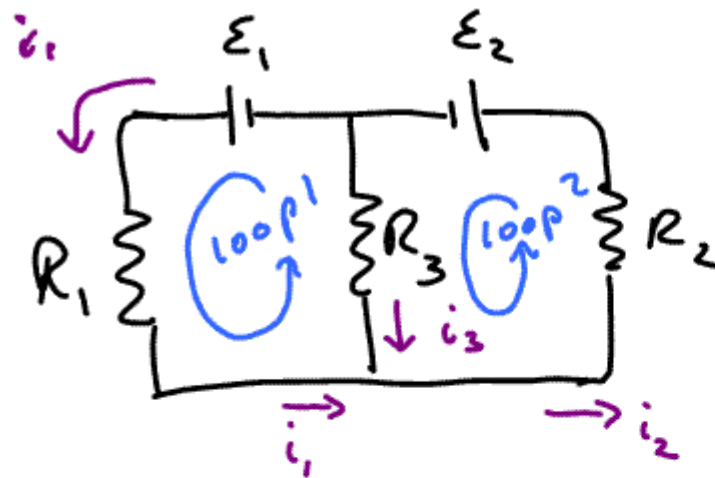

Know ϵ_1, ϵ_2
 R_1, R_2, R_3


Solve for current
 thru out
 circuit

Kirchoff's 2ND rule $i_1 + i_3 = i_2$ (I)


$$\epsilon_1 - i_1 R_1 + i_3 R_3 = 0 \quad \text{(II)}$$

$$-i_3 R_3 - i_2 R_2 - \epsilon_2 = 0 \quad \text{(III)}$$

DC - RC circuits

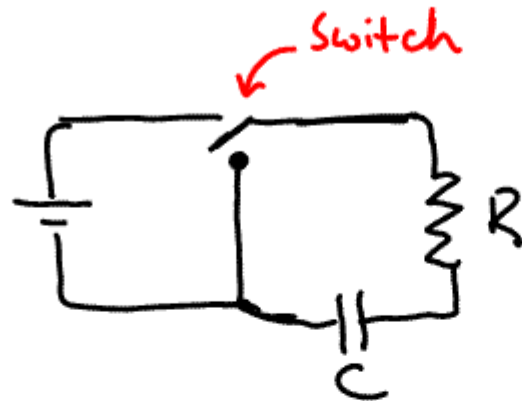

Switch up

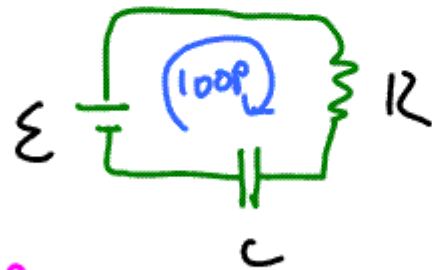

$$\Sigma V = 0$$

$$\Sigma -iR - \frac{q}{C} = 0$$

differential eqn



$$\Sigma = \frac{dq}{dt} R + \frac{q}{C}$$

$$q = C \epsilon (1 - e^{-t/RC})$$

