

Physics 142 - November 6, 2007

■ Exam 2 on Thursday

- Q+A Session B+L106

Wednesday 3:30 - 5:00

- checking about running it from 4-5:30 instead

■ Presentation groups

- Elect spokesperson

- Each group to meet briefly w/ me before Thanksgiving break.

Induction

$$\mathcal{E} = \oint \vec{E} \cdot d\vec{l} = - \frac{d\Phi_m}{dt}$$

↑ Induced EMF

$$\Phi_m \equiv \int_{\text{loop}} \vec{B} \cdot d\vec{A}$$

Faraday's Law

Last
Time

Lenz's Law - An induced current in a closed conducting loop will appear in such a way as to oppose the change that created it.

Gives direction of induced effect



$$\Phi_m = L i$$

$L \equiv$ CONSTANT OF
Self-inductance

$$\mathcal{E} = - \frac{d\Phi_m}{dt} = - L \frac{di}{dt}$$



units Henrys

$$\mathcal{E} = - L \frac{di}{dt}$$



$$\Phi_{m(2)} = M i_{(1)}$$

$$\Phi_{m(1)} = M i_{(2)}$$

SAME "M"
Cross-Talk dictated
by Geometry

$M \equiv$ CONSTANT OF Mutual inductance

$$\mathcal{E}_{(2) \text{ by } (1)} = - M \frac{di_{(1)}}{dt}$$

$$\mathcal{E}_{(1) \text{ by } (2)} = - M \frac{di_{(2)}}{dt}$$

unless problem is specifically about
mutual inductance ... usually treat
inductance in a circuit as self-inductance

Energy density in the fields:

$u_E = \frac{\epsilon_0 E^2}{2}$	$u_B = \frac{B^2}{2\mu_0}$
----------------------------------	----------------------------


general — says nothing about
circuits or sources
or boundary
conditions!

Energy in Inductor

$$U = \frac{1}{2} L I^2$$

similar to $U_{\text{capacitor}} = \frac{1}{2} C V^2$


LR circuit

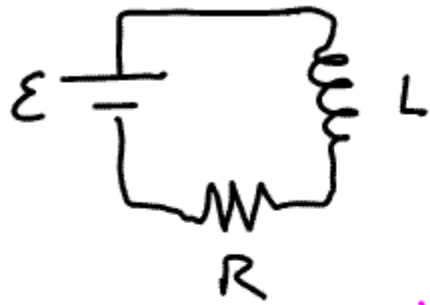

$$\mathcal{E} - L \frac{di}{dt} - iR = 0$$

$$i = \frac{\mathcal{E}}{R} (1 - e^{-tR/L}) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L})$$

small τ_L

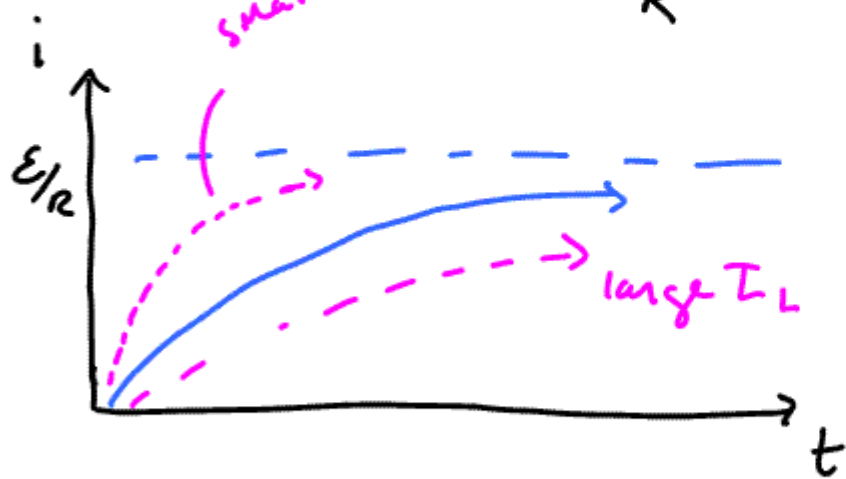


Induction time
constant

$$\tau_L = \frac{L}{R}$$

$V = iR$ for V across R

$$V = \mathcal{E} (1 - e^{-tR/L}) = \mathcal{E} (1 - e^{-t/\tau_L})$$


Remove EMF, Short L across R

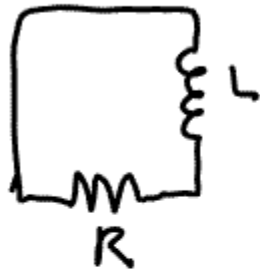


$$0 = iR + L \frac{di}{dt}$$

$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$

After i reaches value of \mathcal{E}/R

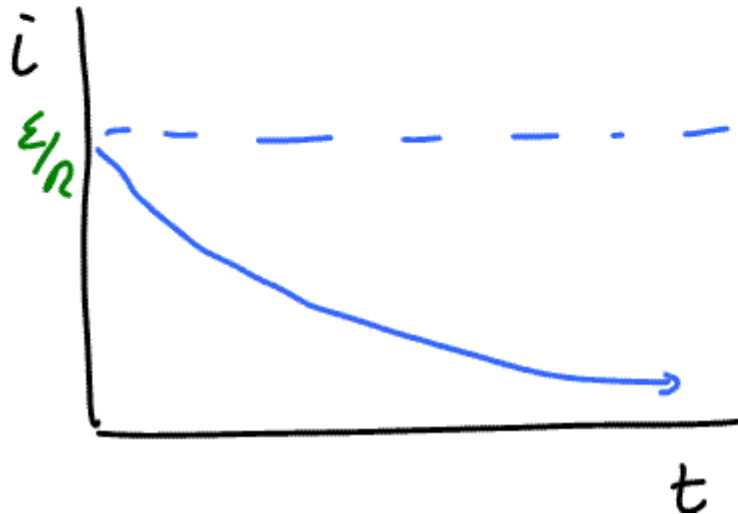

LC circuit

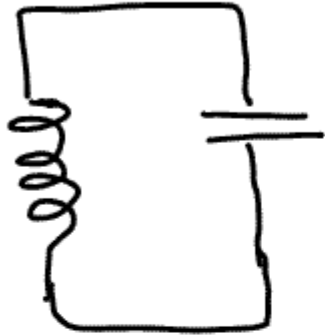

$$U = U_B + U_E = \frac{1}{2} L i^2 + \frac{q^2}{2C}$$

R in circuit $\rightarrow 0$

$$\frac{dU}{dt} = 0 = \frac{1}{2} L 2i \frac{di}{dt} + \frac{2q}{2C} \frac{dq}{dt}$$

$$0 = L \frac{di}{dt} + \frac{q}{C}$$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

diff eqn

SHM

$$m \frac{d^2 x}{dt^2} = -kx$$

same form

$$q(t) = Q \cos(\omega t + \phi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$

HARMONIC

Energy Flow


$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$


Energy
in
Capacitor
or E field

$$i(t) = \frac{dq(t)}{dt} = -Q\omega \sin(\omega t + \phi)$$


$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \phi)$$

LC Oscillations

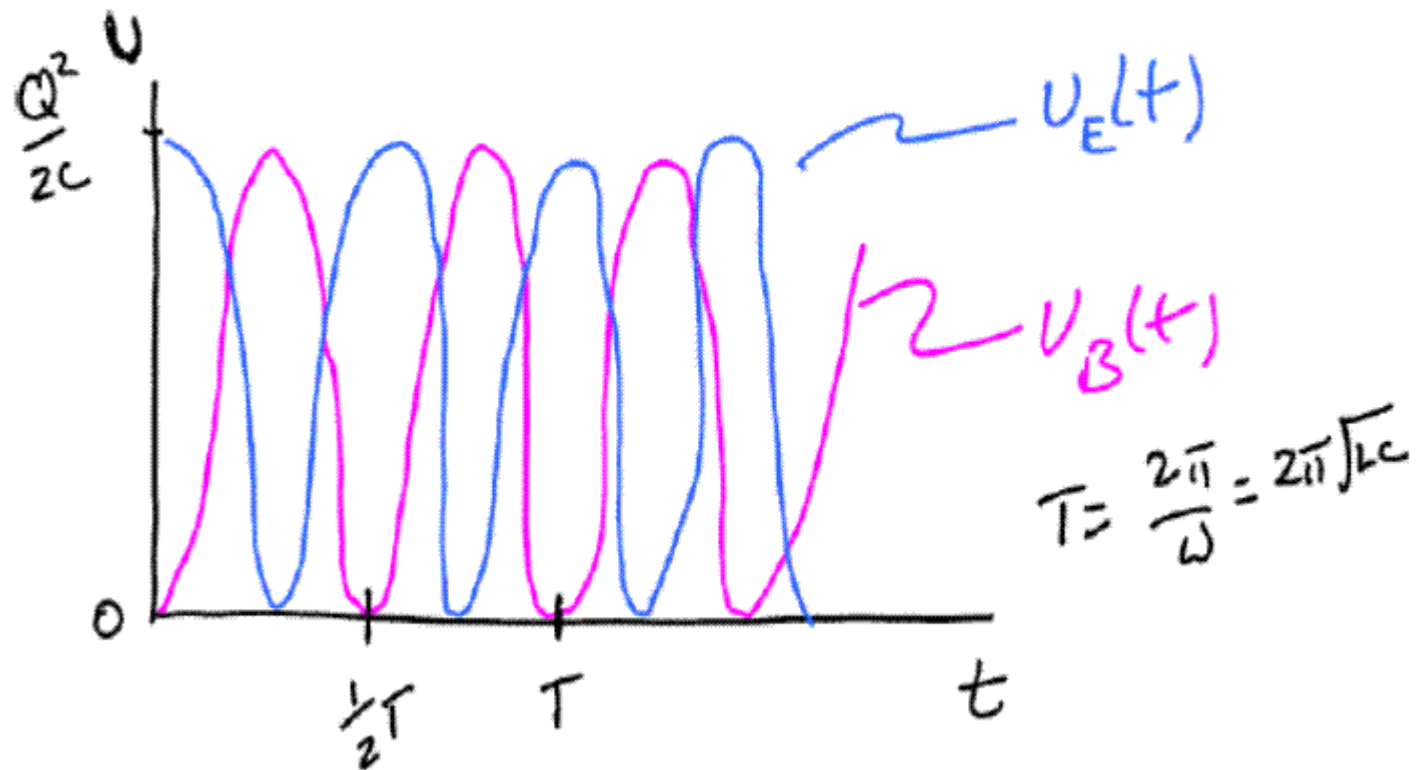

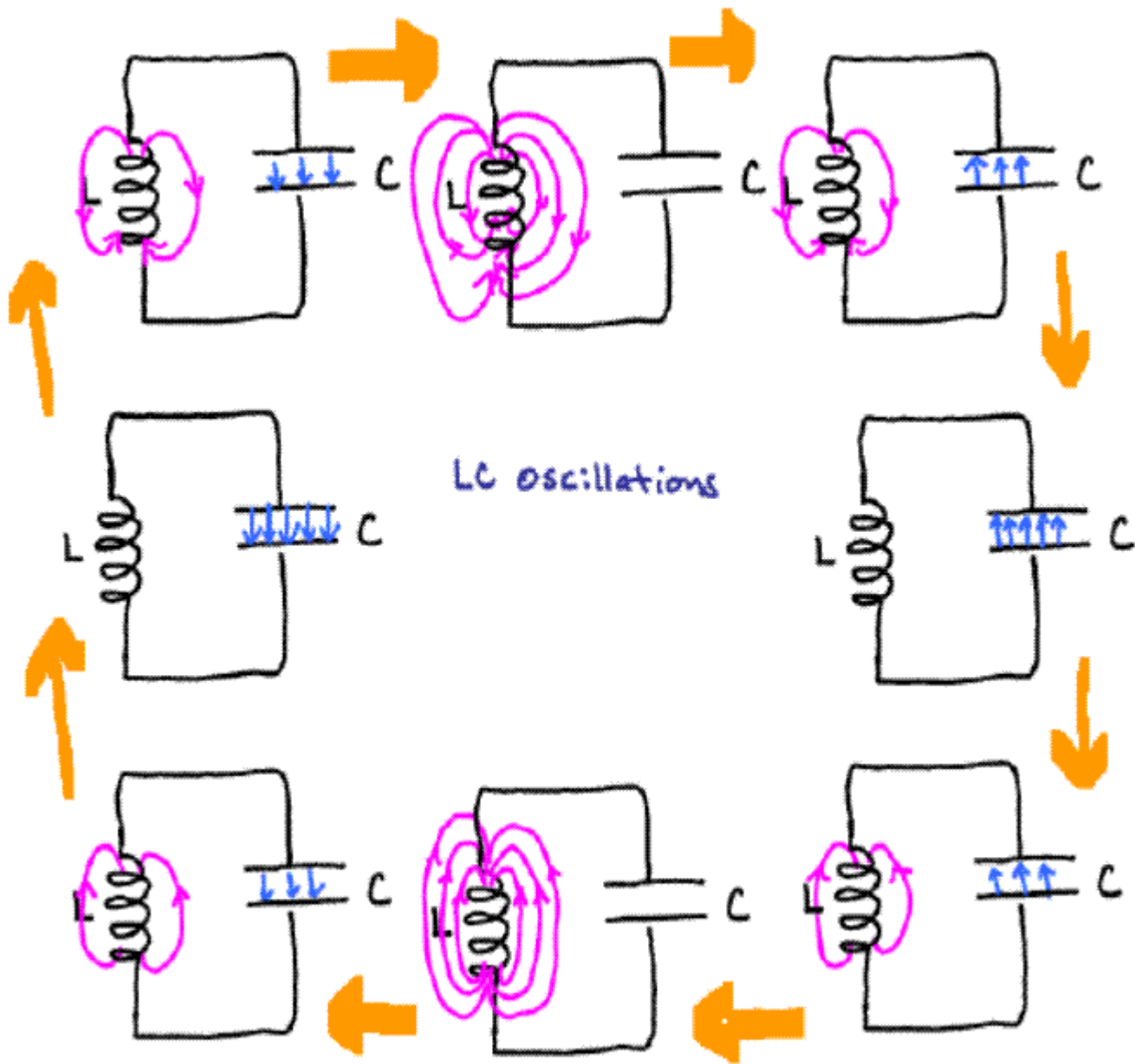


AC Circuits

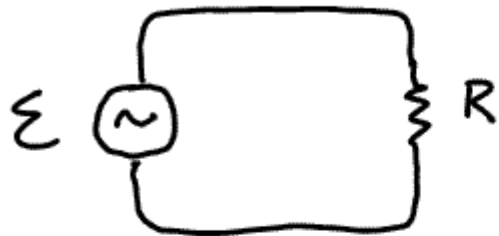

I is in phase with \mathcal{E}
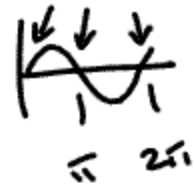
$$\mathcal{E} = \mathcal{E}_{\max} \sin \omega t$$




Kirchoff $\mathcal{E} - IR = 0$

$$I = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{\max} \sin \omega t}{R}$$

Power (instantaneous)
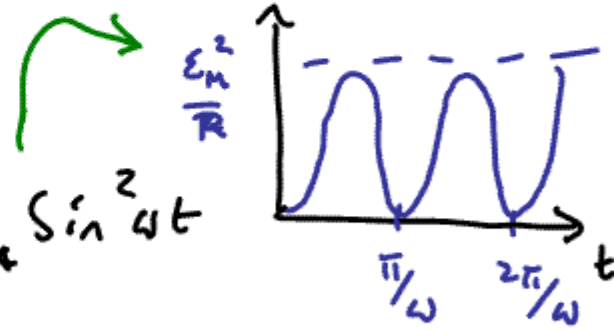
$$P = IV = I\mathcal{E} = \frac{\mathcal{E}_{\max}^2}{R} \sin^2 \omega t$$



Average Power

$$\bar{P} = \frac{\mathcal{E}_{\max}^2}{2R}$$

$$\langle \sin^2 \rangle \sim \frac{1}{2}$$