
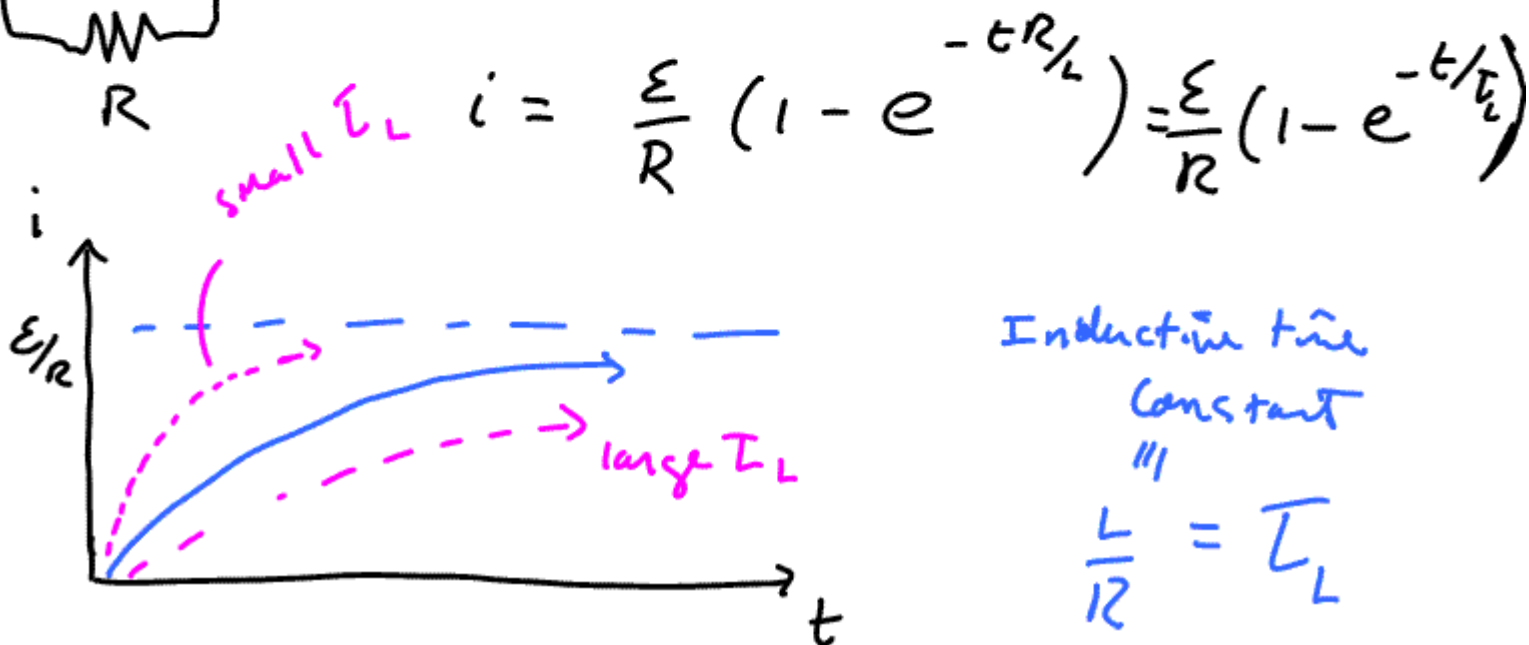


Physics 142 - November 13, 2007

Hope to return exam on Thursday


Last Time -

LR circuit

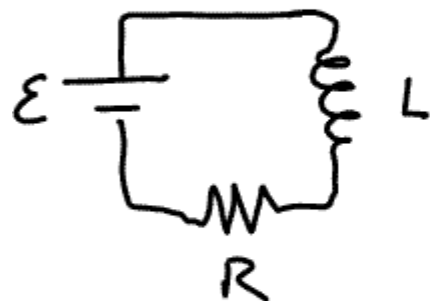



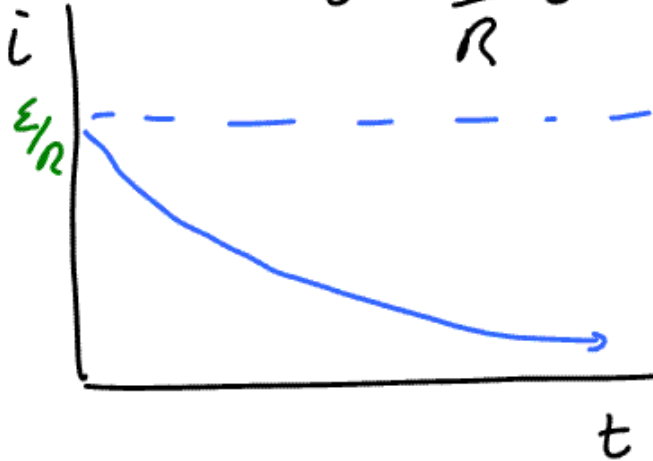
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



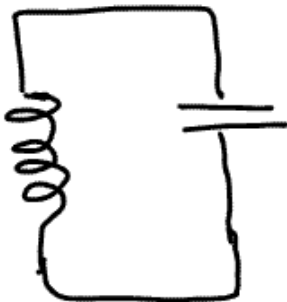LC circuit $U = U_B + U_E = \frac{1}{2} L i^2 + \frac{q^2}{2C}$



Look at
 $\frac{dq}{dt}$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

diff eqn

$$q(t) = Q \cos(\omega t + \phi)$$


$$\omega = \frac{1}{\sqrt{LC}}$$

HARMONIC

Energy Flow

$$U_E = \frac{q^2}{2C} = \frac{Q^2 \cos^2(\omega t + \phi)}{2C}$$
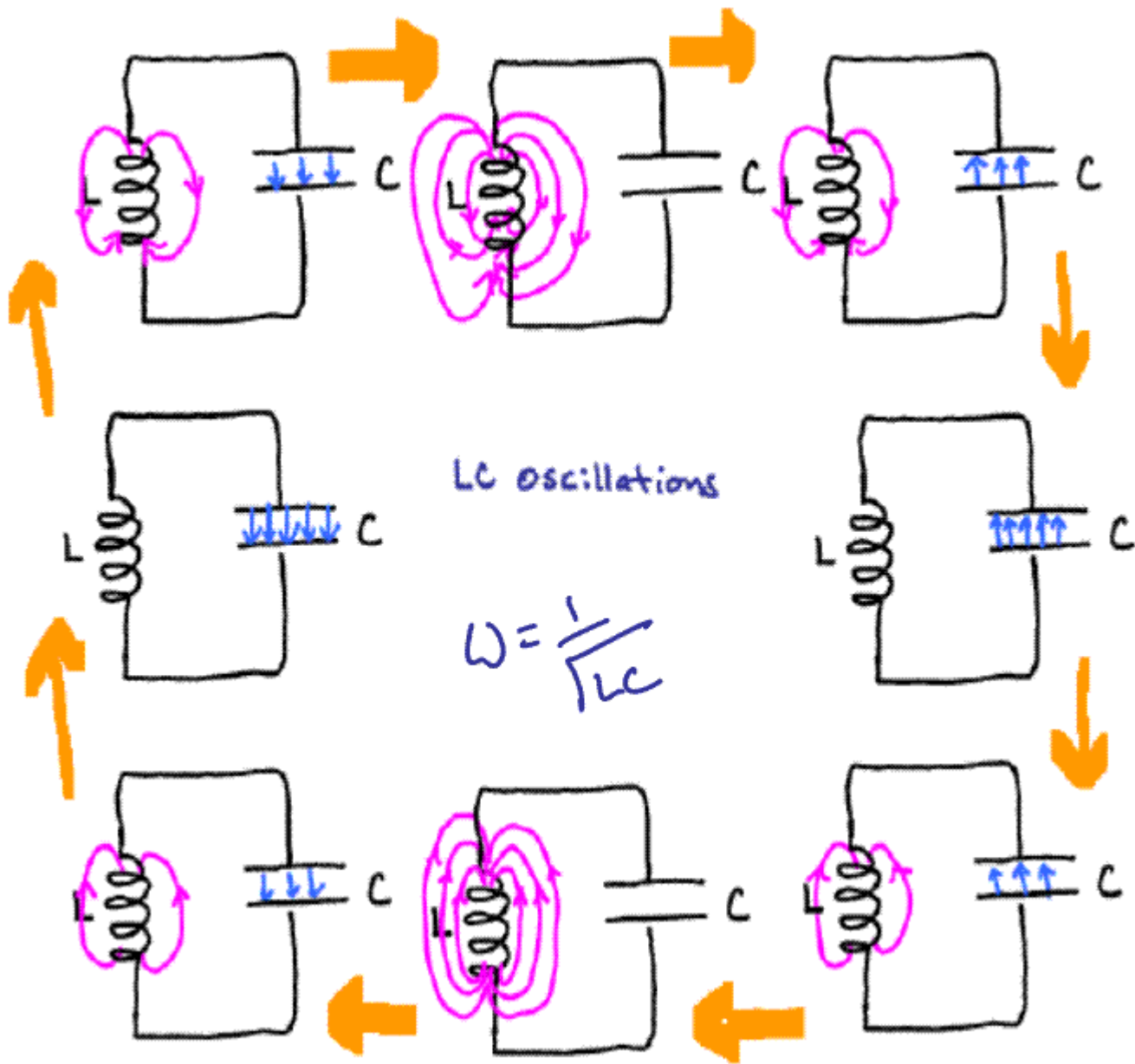
$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \phi)$$



AC Circuits



$$\mathcal{E} = \mathcal{E}_{\text{max}} \sin \omega t$$


Kirchoff

$$\mathcal{E} - IR = 0$$

$$I = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{\text{max}} \sin \omega t}{R}$$


Instantaneous
Power
Dissipation
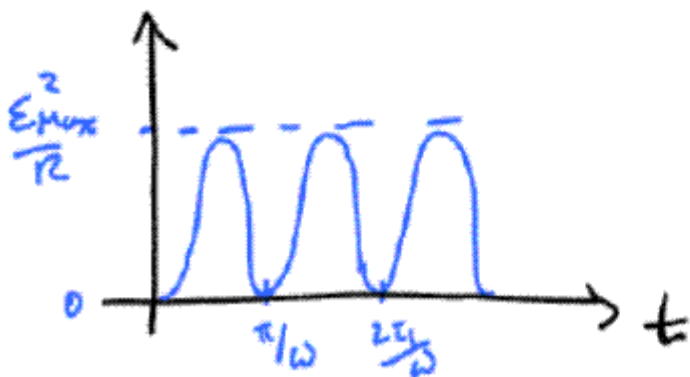
$$P = IV = I\mathcal{E} = \frac{\mathcal{E}_{\text{max}}^2}{R} \sin^2 \omega t$$



$$\overline{\sin^2 \theta} \rightarrow \frac{1}{2}$$
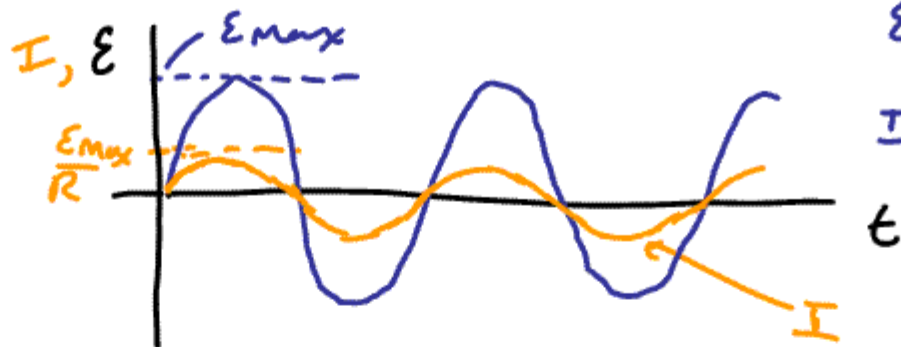
$$\text{Ave Power} \quad \bar{P} = \frac{\mathcal{E}_{\text{max}}^2}{2R}$$



$$\varepsilon = \varepsilon_{\max} \sin \omega t$$


$$I = \frac{\varepsilon_{\max}}{R} \sin \omega t$$

In phase



$$Q = C\varepsilon = C\varepsilon_{\max} \sin \omega t$$
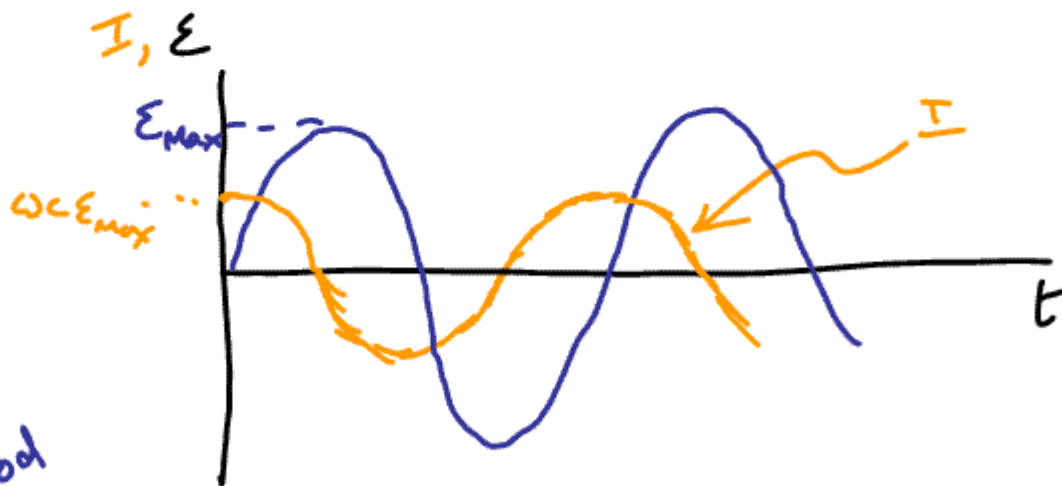
$$I = \frac{dQ}{dt} = \omega C\varepsilon_{\max} \cos \omega t$$




I "leads" ε MF
by $\frac{1}{4}$ period
cycle

$$V \sim IR$$

$$\frac{1}{\omega C} I = \epsilon_{\max} \cos \omega t$$

plays role of RESISTANCE in capacitive AC circuit

$X_C \equiv$ Capacitive Reactance

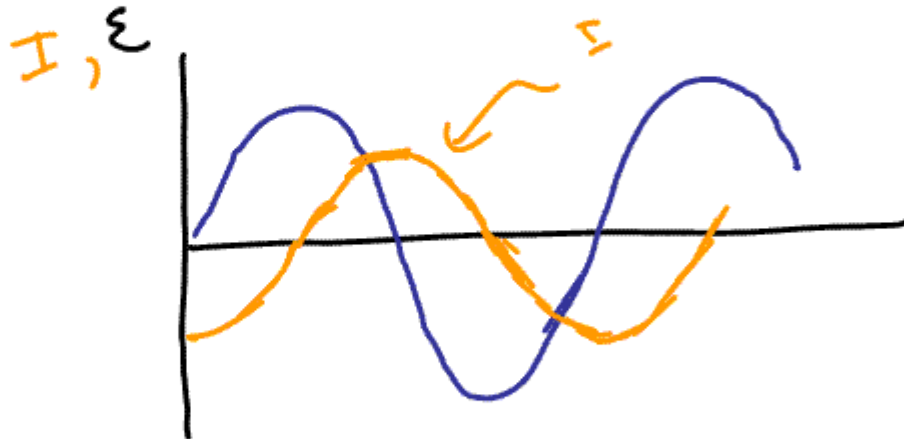

$$\epsilon - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = \frac{\epsilon_{\max} \sin \omega t}{L}$$


$$I = - \frac{\epsilon_{\max} \cos \omega t}{\omega L}$$

I "lags" EMF by $\frac{1}{4}$ cycle

$\omega L \equiv X_L \equiv$ Inductive Reactance

$$I \chi_L = - \epsilon_{\max} \cos \omega t$$

Think \curvearrowright $v = IR$

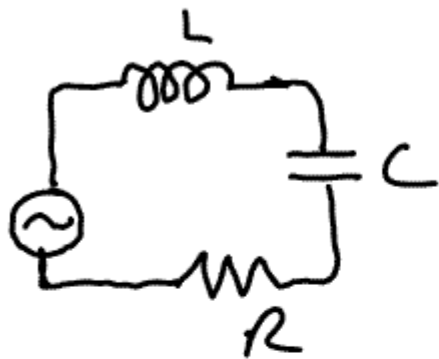

LRC circuit

$$\epsilon = \epsilon_{\max} \sin \omega t$$

$$I = I_{\max} \sin(\omega t + \phi)$$

phase ϕ (?)

?

$$\epsilon = \underbrace{\Delta V_R}_{R I_{\max} \sin(\omega t + \phi)} + \underbrace{\Delta V_C}_{-\chi_C I_{\max} \cos(\omega t + \phi)} + \underbrace{\Delta V_L}_{\chi_L I_{\max} \cos(\omega t + \phi)}$$

$$R I_{\max} \sin(\omega t + \phi)$$

$$-\chi_C I_{\max} \cos(\omega t + \phi)$$

$\frac{1}{4}$ cycle behind ϵ, I



Math, Trig ID's

look at text

$$\tan \phi = \frac{\chi_L - \chi_C}{R}$$

$$I_{\text{Max}} = \frac{\mathcal{E}_{\text{Max}}}{\sqrt{R^2 + (\chi_L + \chi_C)^2}}$$

\equiv Impedance $\equiv Z$

$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

plays Role of
"R" in
LRC
circuit


have \sim at freq ω

look at $\omega \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$



$$Z \rightarrow \sqrt{R^2 + \left(\frac{L}{\sqrt{LC}} - \frac{\sqrt{LC}}{C}\right)^2}$$

$\downarrow 0$

\rightarrow maximizes I

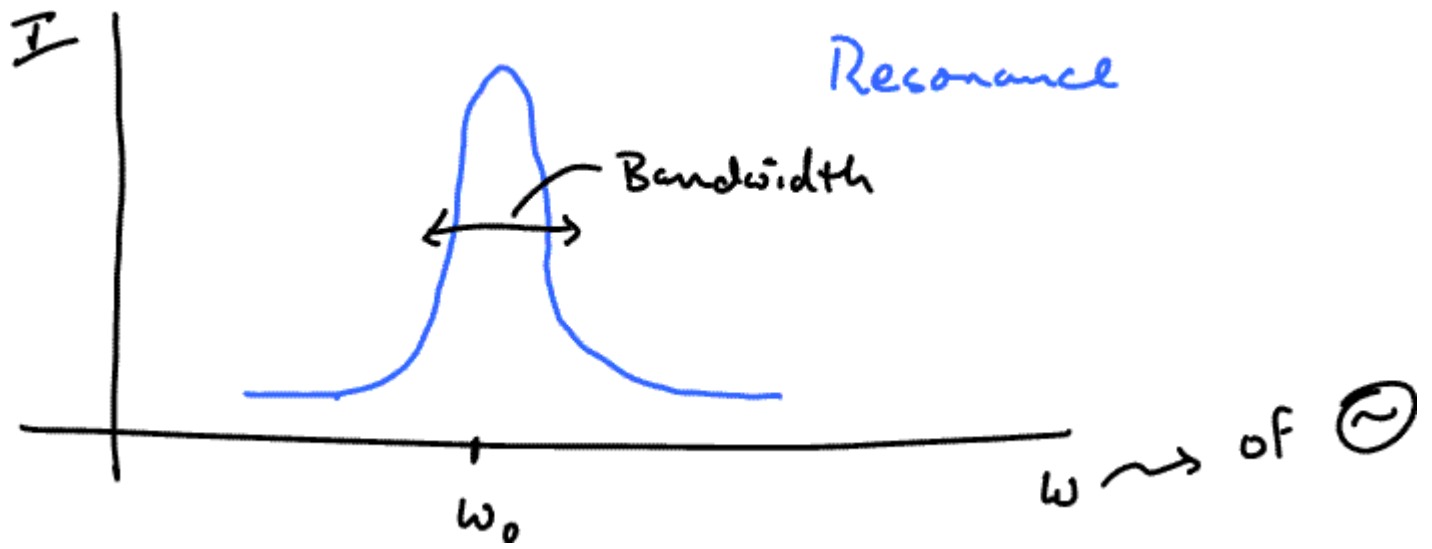

Magnetic fields in matter

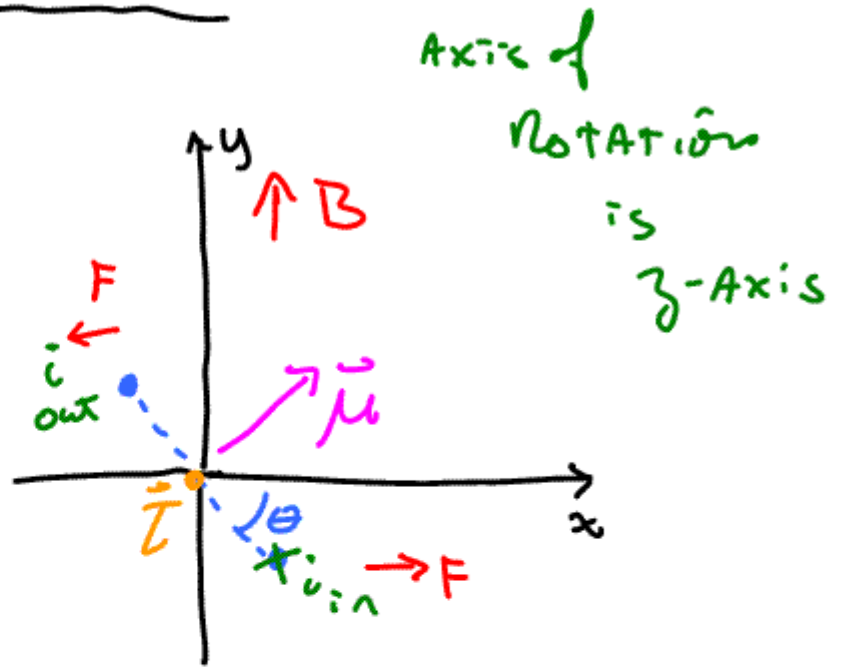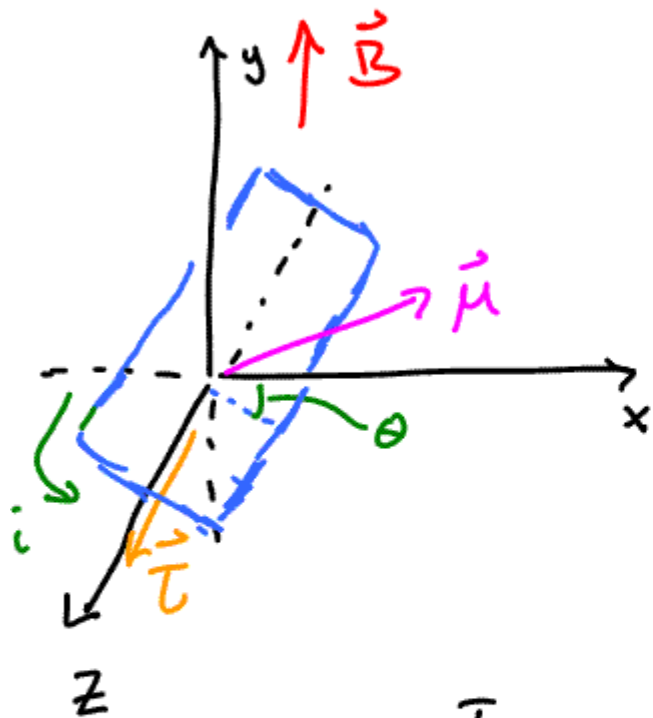

Axis of rotation is z-axis

Torque on current loop = $\vec{\mu} \times \vec{B} = \vec{\tau}$
Dipole



Dipole magnetic field


Define Magnetic Moment of current loop $\equiv I A = |\vec{\mu}|$

cross sect. Area of loop

Paramagnetic



Diamagnetic

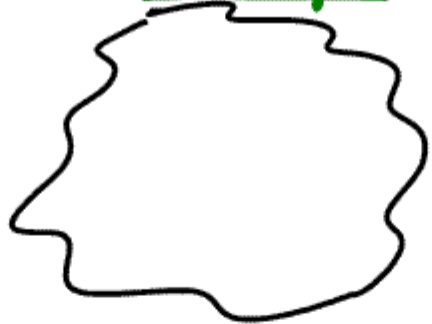

No dipole

Ferromagnetic



Will come back to this
...