

Physics 142 - September 30, 2008

■ Exam 1 - Oct 7 0800-0920 B+L 109
NOT Oct 2 during class time

- Calculators
- 1 3x5 index card (both sides) formulas
- Past P142 exams
- formula sheet + integral tables supplied
- material coverage

■ START up to Dielectrics

■ P.S. 1-4 (except probs 13-15 of PS4)

■ Workshops 1-4

■ Lectures Thru start of Dielectrics today

■ Text chaps 22-26.2, 1st page of 26.4

Graded
P.S.
Available
thru P.S. 3

Last Time -




Potential
(D.Fference) $\propto Q$

$$V = QC$$

$C \equiv$ capacitance (Farads \equiv mks unit)

Depends on geometry

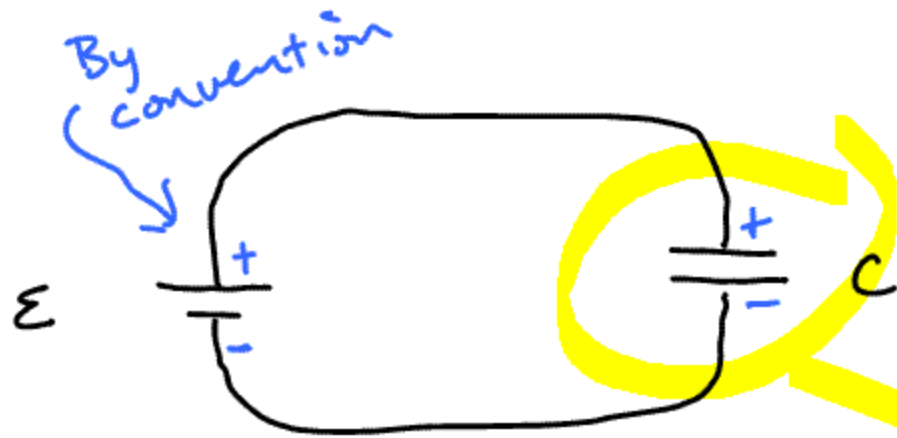


each plate

$Q \equiv \text{charge}$

$A \equiv \text{Area}$

$$V = Q/A$$

Gaussian surface \sim Area $\sim A$

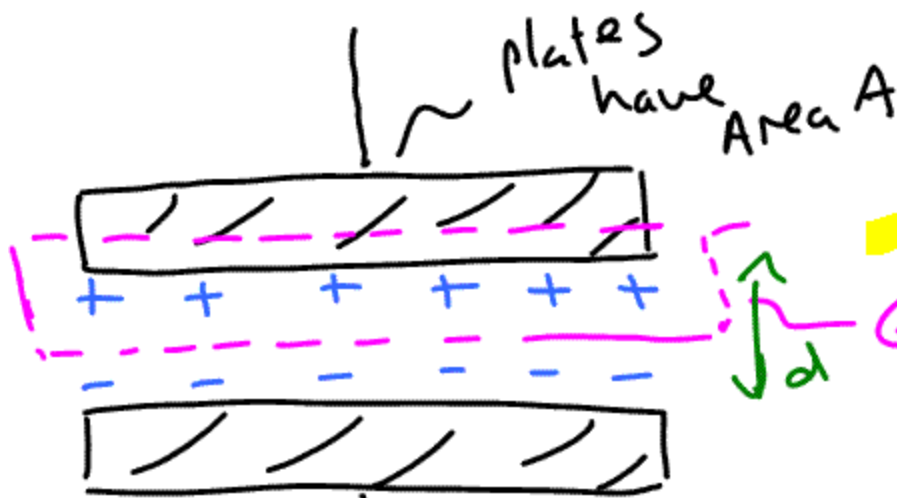

Find expression for capacitance of system

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{enc}}}{\epsilon_0}$$



$$|\vec{E}| A = \frac{\sigma A}{\epsilon_0}$$


↑
of bottom of box

$$V = \frac{W}{q} = \frac{Fd}{q} = Ed$$

for // plates
 $|\vec{E}| = \frac{\sigma}{\epsilon_0}$

$$C = \frac{Q}{V} = \frac{\sigma A}{Ed} = \frac{A\epsilon_0}{d}$$

only geometry

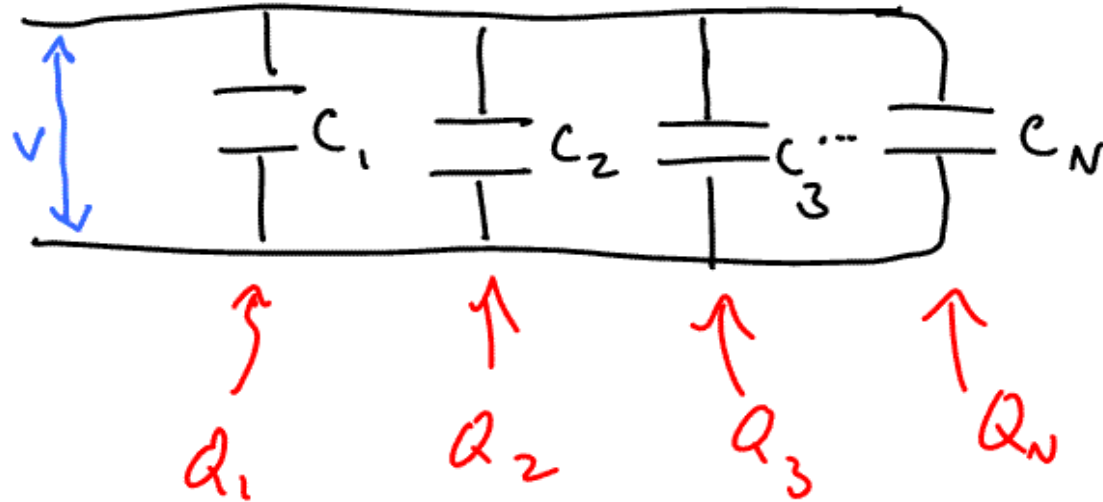

Capacitors
in
Parallel

$$Q_{\text{TOT}} = Q_1 + Q_2 + \dots + Q_N$$

$$Q_{\text{TOT}} = C_{\text{TOT}} V$$

↑
Total capac. of circuit

$$Q_1 = C_1 V$$


$$Q_2 = C_2 V$$

$$Q_N = C_N V$$

$$C_{TOT} V = C_1 V + C_2 V + \dots + C_N V$$


$$C_{TOT} = C_1 + C_2 + \dots + C_N = \sum C_i$$

$C = \sum C_i$ capacitors
in
Parallel

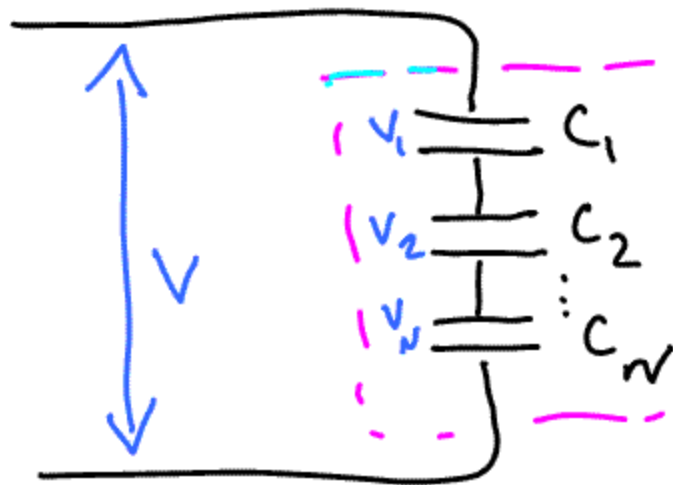

Capacitors
in
Series

$$C_{TOT} V = Q_{TOT}$$

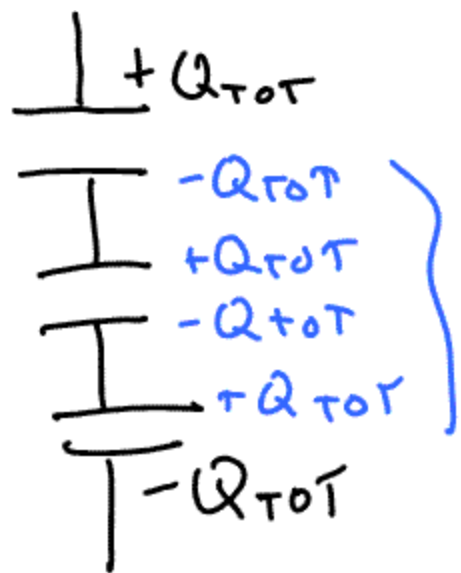

chg induced

$$C_1 V_1 = Q_{TOT}$$

$$C_2 V_2 = Q_{TOT}$$

$$C_N V_N = Q_{TOT}$$

$$V = V_1 + V_2 + \dots + V_N$$


$$C_{TOT} V = Q_{TOT}$$

$$\frac{Q_{TOT}}{C_{TOT}} = \frac{Q_{TOT}}{C_1} + \frac{Q_{TOT}}{C_2} + \dots + \frac{Q_{TOT}}{C_N}$$

$$\frac{1}{C_{TOT}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

$$\frac{1}{C} = \sum_i \frac{1}{C_i} \quad \text{capacitors in series}$$


Time dependence

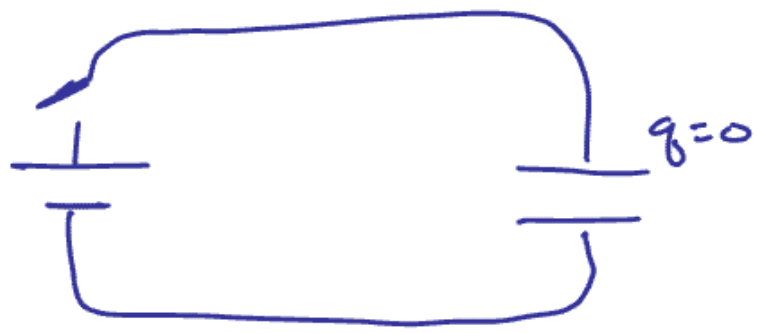

at moment switch is closed capacitor begins to charge

Moment later

$$V = \mathcal{E}MF$$

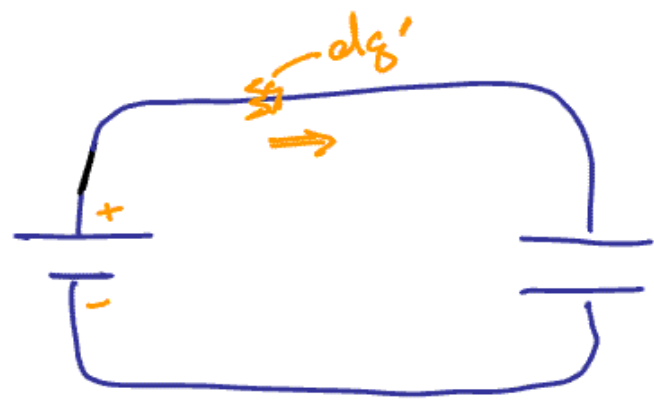

$$q', V'$$

$$q' = CV'$$

$$dW = v' dq'$$

$$q' = c v' \quad \uparrow \text{ geometry}$$


$$dW = \frac{q'}{c} dq' \quad Q = CV$$

$$W = \int_0^Q \frac{q'}{c} dq' = \frac{1}{c} \frac{Q^2}{2} = \frac{c^2 v^2}{c^2} = \frac{1}{2} c v^2$$

Energy Stored by Capacitor

Work it takes to charge a capacitor

$$= \frac{1}{2} c v^2 = \frac{Q^2}{2c}$$

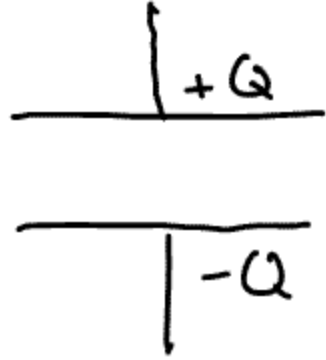

where is the energy?

→ in Electric field

Energy density of electric field

|||

$$u_E = \frac{U_{\text{TOT Energy}}}{\text{Vol. bet. plates}} = \frac{\frac{1}{2} CV^2}{dA}$$

$$C \text{ // plates} = \frac{A\epsilon_0}{d}$$

$$\frac{1}{2} \frac{A\epsilon_0}{d} V^2 \frac{1}{dA}$$

$$V \sim Ed$$

$$u_E = \frac{\epsilon_0 V^2}{2d^2} = \epsilon_0 \frac{|E|^2 d^2}{2d^2}$$

$$u_E = \frac{\epsilon_0}{2} |E|^2$$


→ general

From a particular geometry that is easy to analyze and understand, we've found an expression for the energy density in electric field.

Final expression contains nothing specific to the particular example chosen.

⇒ This is a general result

Electric fields carry energy

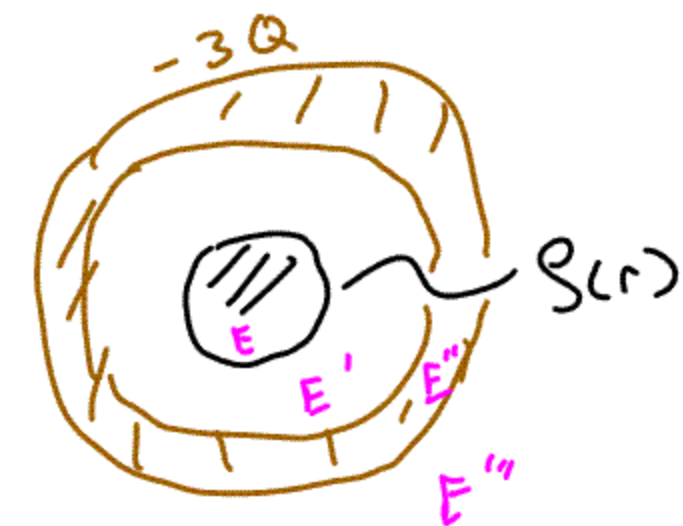

Some
"system"

can look at any system
and solve for $|\vec{E}|$.

Once you know $|\vec{E}|$
everywhere you can
calculate the total
energy of the system as

TOTAL energy

$$U = \int_{\text{Vol}} u_E dv$$