

Physics 142 - October 9, 2008

- Presentation topic list

Return to me next Tuesday

Last Time -

- Resistance

$$V = IR$$

Ohm's Law

Resistance

unit
 Ω

Impedes electrons "Looking" for love 

Pass current thru resistor - Energy lost as heat or light

Power dissipated

$$P = iV = i^2 R = i^2 R$$

$$P = i^2 R$$

Mostly

$$V = iR$$

$$i = V/R$$

$$P = \frac{V^2}{R}$$


Resistors in series

$$R = \sum_i r_i$$

Resistors in parallel

$$\frac{1}{R} = \sum_i \frac{1}{r_i}$$

Last Time

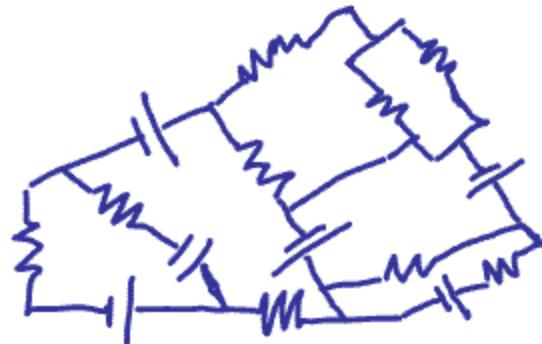

suppose you meet
a circuit
in a dark
Alley one
night ...

... And the electrons are
Not looking for love ...

Kirchoff's Rules:

- ① $\sum V = 0$ around closed loop in circuit
- ② current is conserved at any branch point in circuit

-
- use these rules to create N independent equations to solve for N unknowns
 - Choose independent loops
 - Use sign conventions consistently + with care


convention [told This is opposite that of ECE 210]

↳ no matter if consistent

Choose currents in each branch (arbitrary)

Sum ΔV across each circuit component as you go around an imaginary closed loop in the circuit


ΔV - if  $\Sigma +$ if 

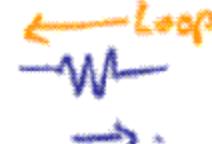$\Delta V +$ if  $\Sigma -$ if 

Get N eqns, N unknowns and solve

Tedious → must be careful and consistent w/ Conventions and Signs

use only independent loops

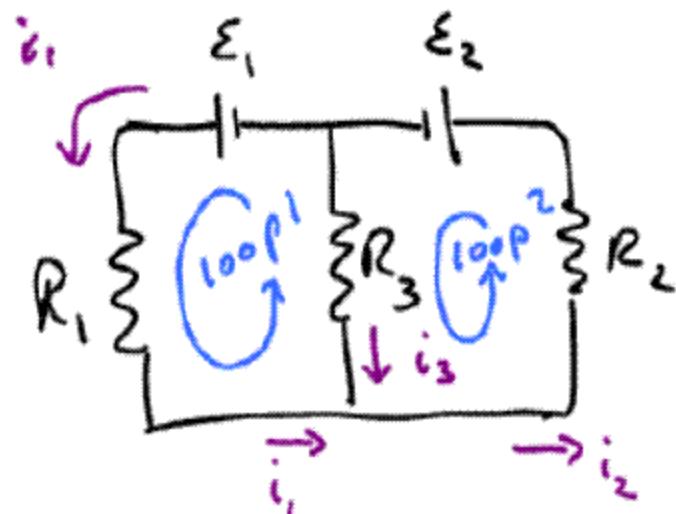

Know E_1, E_2


R_1, R_2, R_3

Solve for current
through
circuit


Kirchhoff's 2nd rule $i_1 + i_3 = i_2$ (I)

$$E_1 - i_1 R_1 + i_3 R_3 = 0 \quad (\text{II})$$

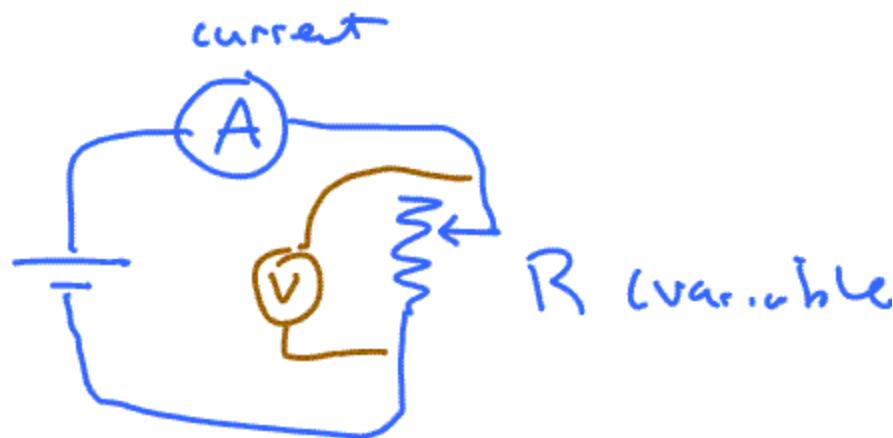
$$-i_3 R_3 - i_2 R_2 - E_2 = 0 \quad (\text{III})$$



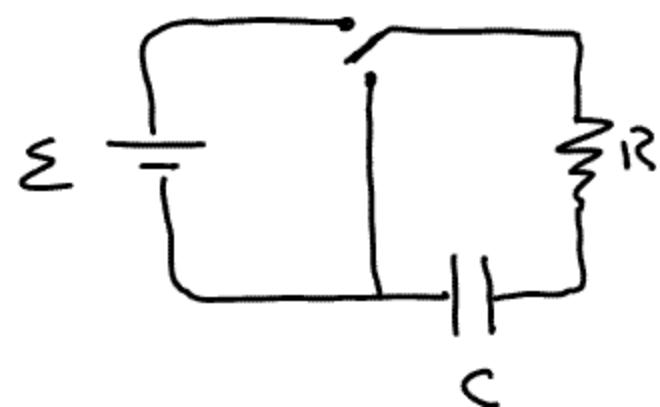$\underbrace{\text{DC circuits}}_{\text{Direct Current}} - \text{RC circuit}$




Switch up — charging RC circuit

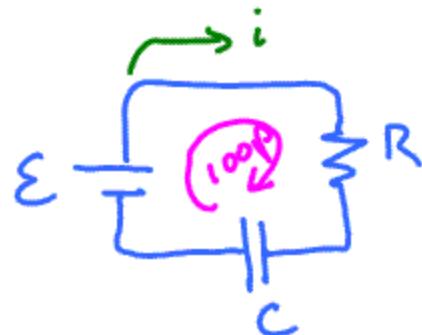

$$\sum V = 0$$

$$\epsilon - iR - \frac{Q}{C} = 0$$





differential equation

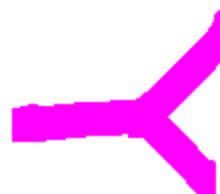


$$\epsilon = \frac{dq}{dt} R + \frac{q}{C}$$

$$q(t) = C\epsilon(1 - e^{-t/RC})$$
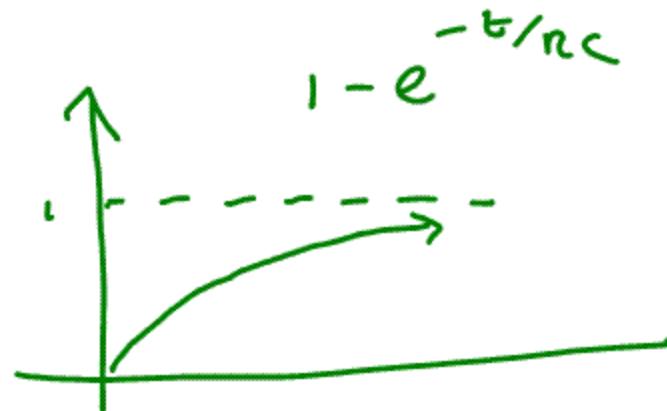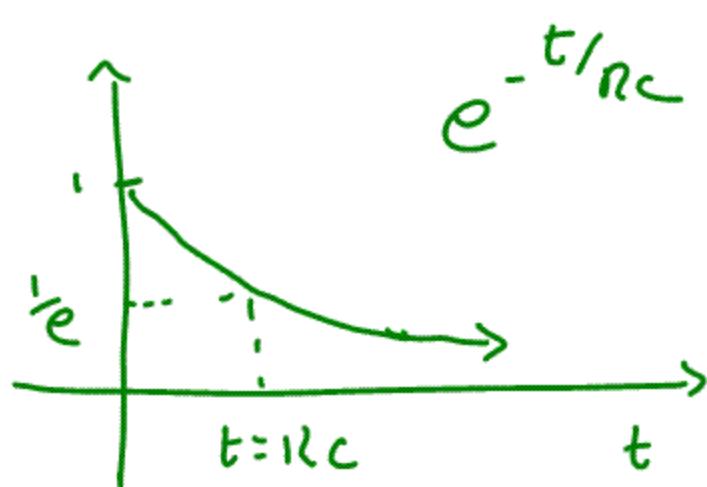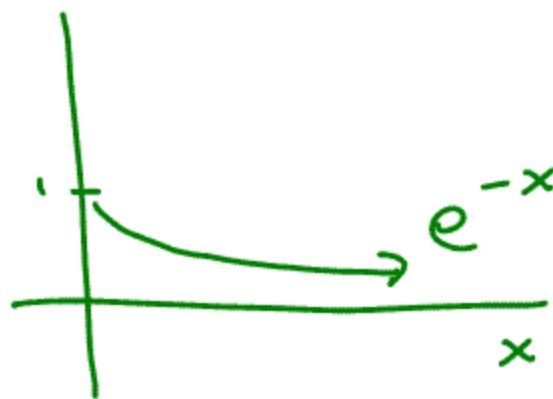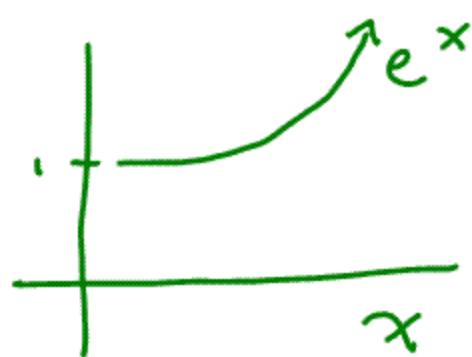
$$g(t) = C\varepsilon \left(1 - e^{-t/RC}\right)$$


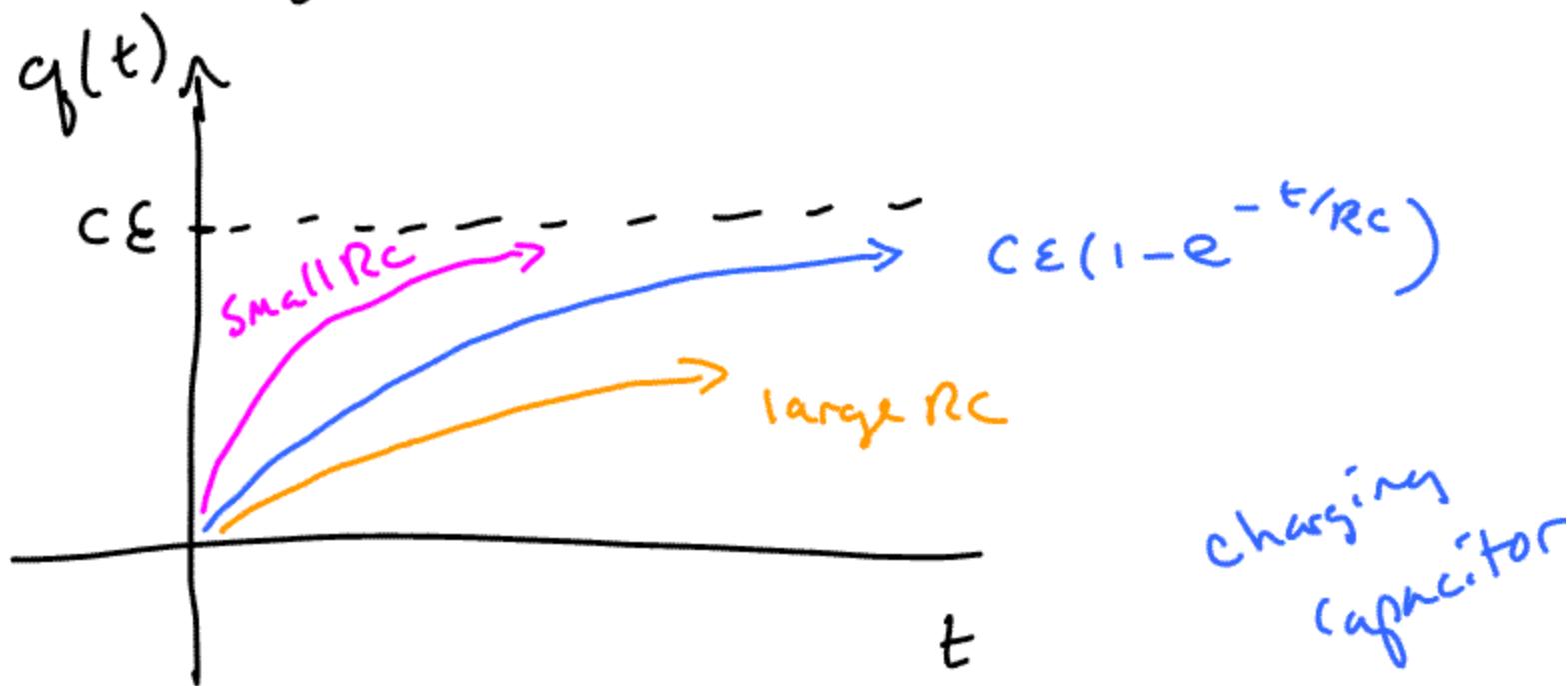
$$q(t) = CE \left(1 - e^{-t/RC} \right)$$



charging
capacitor

$RC \equiv$ time constant of circuit

discharging RC circuit



$$\sum V = 0$$

$$-\frac{dq(t)}{dt} R - \frac{q(t)}{C} = 0$$

$$-\frac{dq(t)}{dt}, R = \frac{q(t)}{C}$$


$$\int_0^t \frac{dt}{RC} = - \int_{q_0}^q \frac{dq}{q}$$

$$\frac{t}{RC} = - \ln \frac{q}{q_0}$$

$$-\frac{t}{R_C} = \ln \frac{g}{g_0}$$

$$e^{-\frac{t}{R_C}} = \frac{g}{g_0}$$

$$g(t) = g_0 e^{-\frac{t}{R_C}}$$

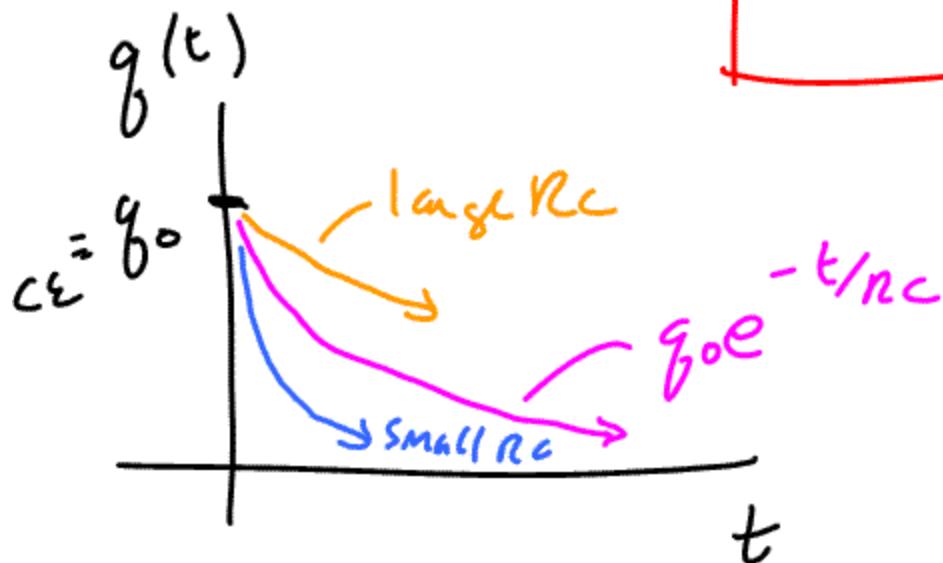

Began chatting about the Special
Theory of Relativity