


Physics 142 - November 6, 2008

- Exam Thurs. Nov. 13, 2008 class time Hoyt
3x5 index card okay
- Q+A session Monday? Expect formula sheet

Last Time -

LR circuit

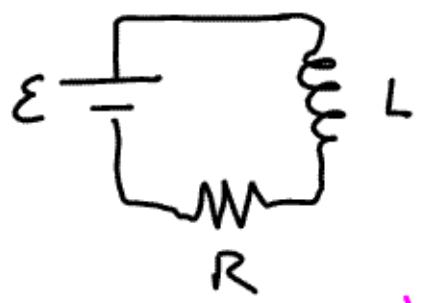
AT START of MP3
Audio file I
mistakenly said
this is the Nov 13
lecture...
meant to
say Nov 6



Ⓐ

small L
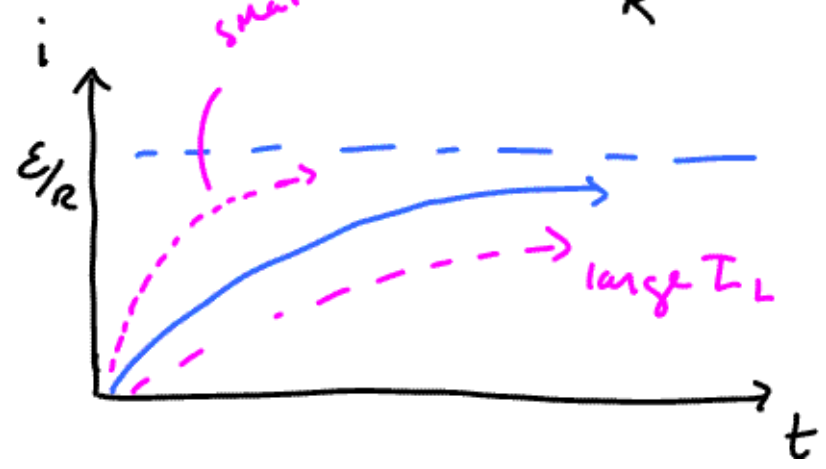
$$i = \frac{\epsilon}{R} (1 - e^{-tR/L}) = \frac{\epsilon}{R} (1 - e^{-t/\tau_L})$$




Induction time
constant
|||


$$\frac{L}{R} = \tau_L$$


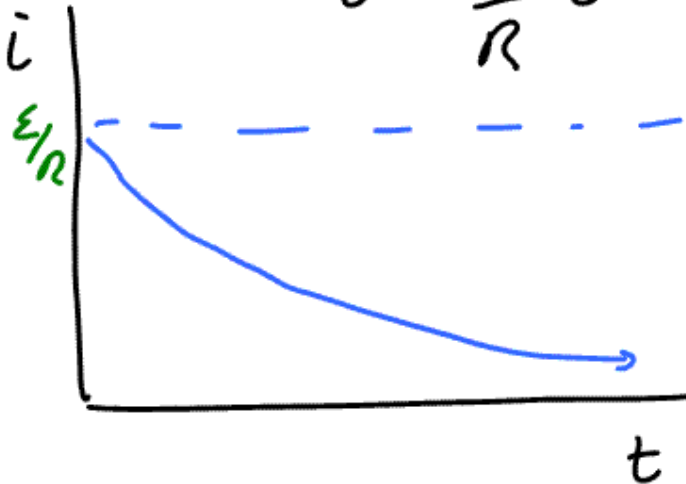
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



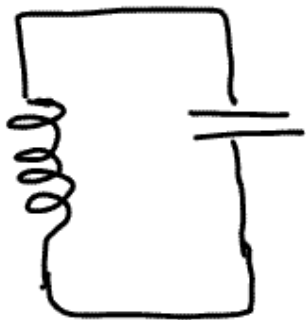LC circuit $U = U_B + U_E = \frac{1}{2} L i^2 + \frac{q^2}{2C}$ (B)



Look at
 $\frac{dq}{dt}$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

(C)

diff eqn

$$q(t) = Q \cos(\omega t + \phi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$


HARMONIC

Energy Flow

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi) \quad \textcircled{A}$$

$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \phi) \quad \textcircled{B}$$

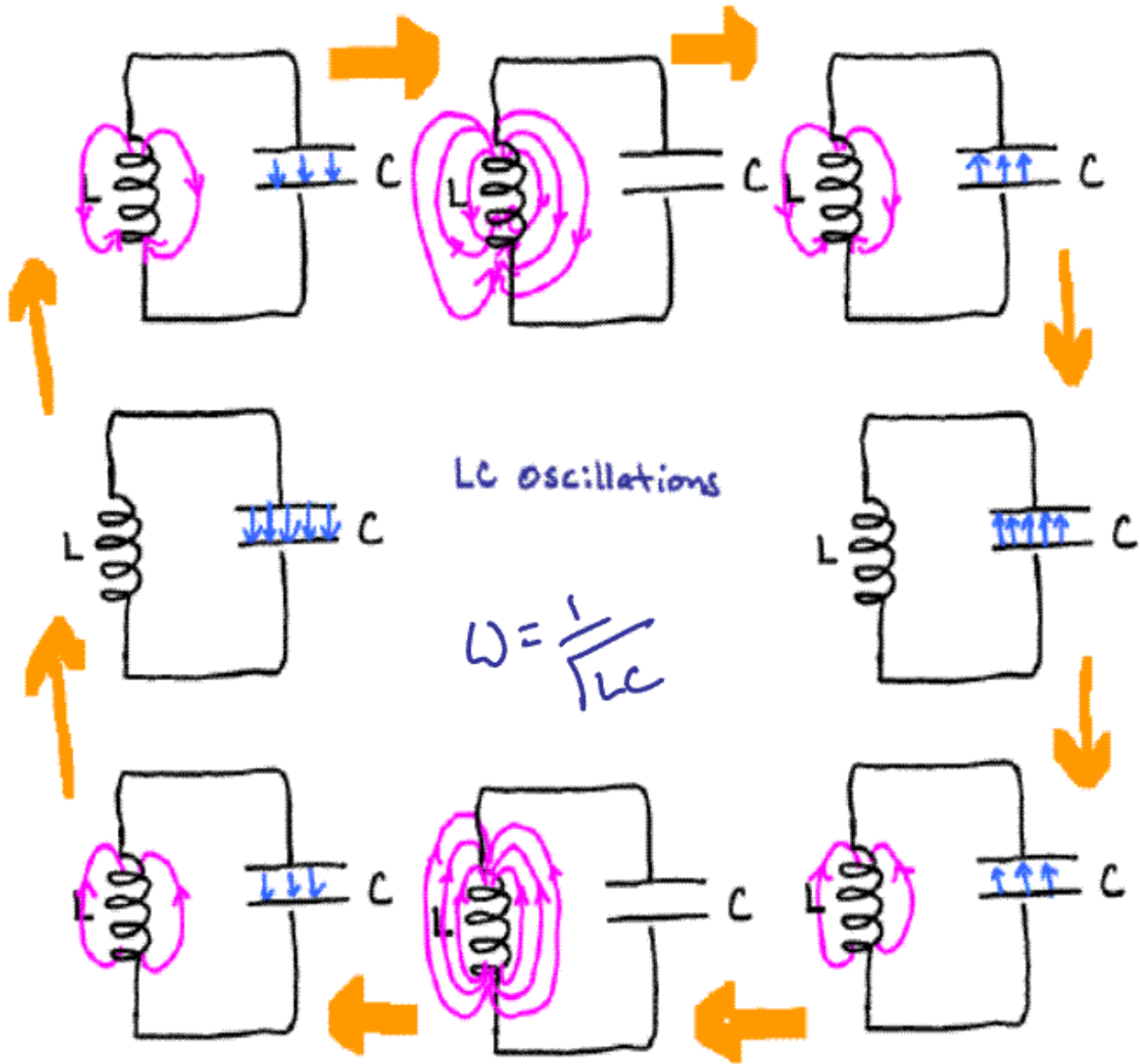Energy flows from capacitor to inductor + back
(E field) (B field)



~ follows Ohm's Treatment

5

AC Circuits



$$\mathcal{E} = \mathcal{E}_{\text{Max}} \sin \omega t$$


Kirchoff

$$\mathcal{E} - IR = 0$$

$$I = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{\text{Max}} \sin \omega t}{R} \quad \textcircled{A}$$



INSTANTANEOUS
POWER
DISSIPATION
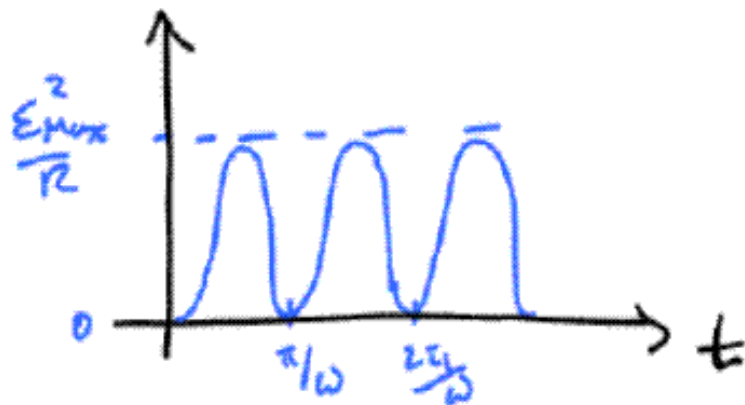
$$P = IV = I\mathcal{E} = \frac{\mathcal{E}_{\text{Max}}^2}{R} \sin^2 \omega t$$



$$\overline{\sin^2 \theta} \rightarrow \frac{1}{2}$$
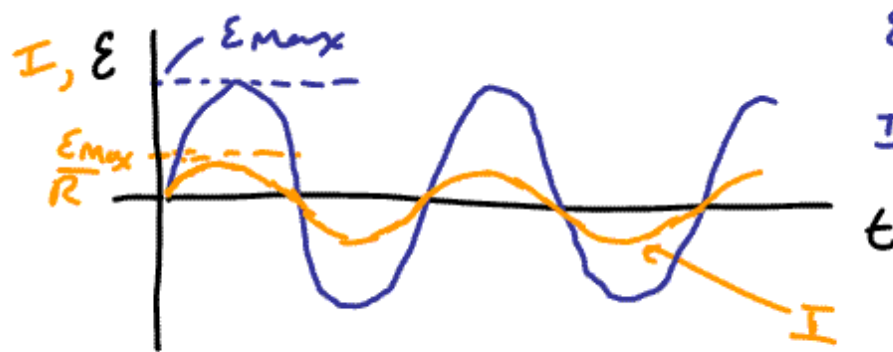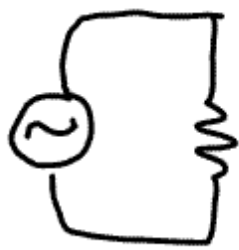
$$\text{AVE POWER} \quad \overline{P} = \frac{\mathcal{E}_{\text{Max}}^2}{2R}$$




$$\epsilon = \epsilon_{max} \sin \omega t$$

$$I = \frac{\epsilon_{max}}{R} \sin \omega t$$

6


In phase

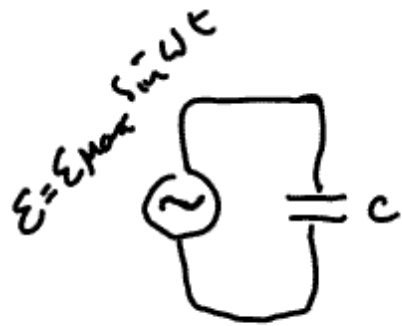

$$\epsilon = \epsilon_{max} \sin \omega t$$

$$Q = C \epsilon = C \epsilon_{max} \sin \omega t$$
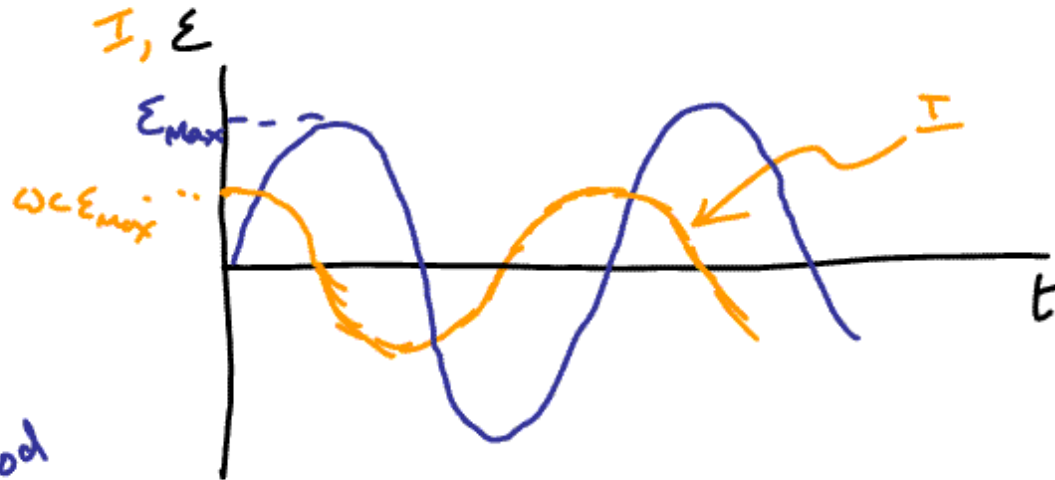
$$I = \frac{dQ}{dt} = \omega C \epsilon_{max} \cos \omega t \quad \text{(A)}$$



I "leads" ϵ MF
by $\frac{1}{4}$ period
cycle


V_{IR}

$$\frac{1}{\omega C} I = \epsilon_{\max} \cos \omega t$$

7

plays role of RESISTANCE in capacitive AC circuit

$X_c \equiv$ Capacitive Reactance

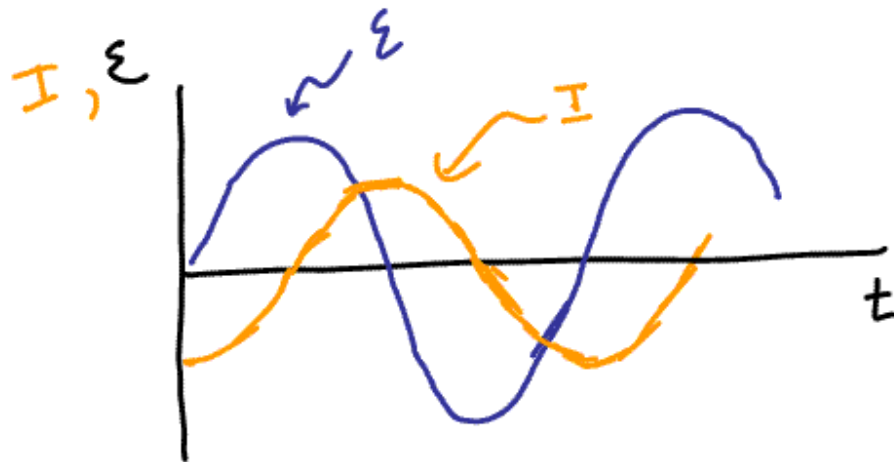

$$\epsilon - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = \frac{\epsilon_{\max} \sin \omega t}{L}$$


$$I = - \frac{\epsilon_{\max} \cos \omega t}{\omega L}$$

I "lags" EMF by $\frac{1}{4}$ cycle

$\omega L \equiv X_L \equiv$ Inductive Reactance

$$I \chi_L = - \epsilon_{\max} \cos \omega t$$

Think $v = IR$ 8

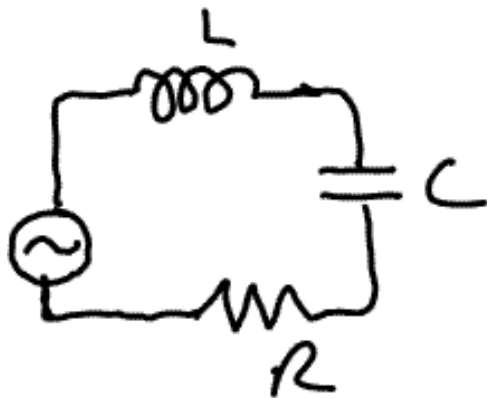




LRC circuit

$$\epsilon = \epsilon_{\max} \sin \omega t$$

$$I = I_{\max} \sin(\omega t + \phi)$$


?

phase?

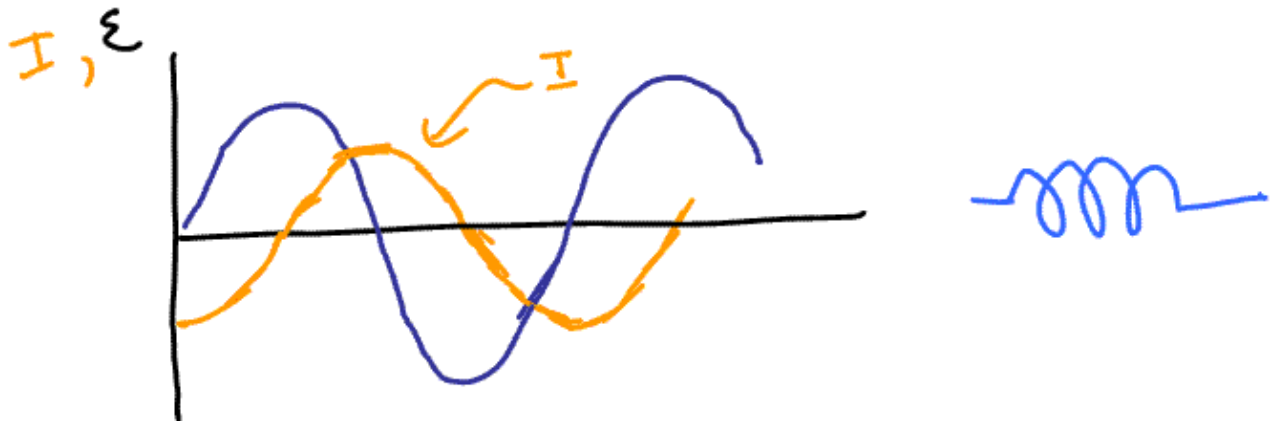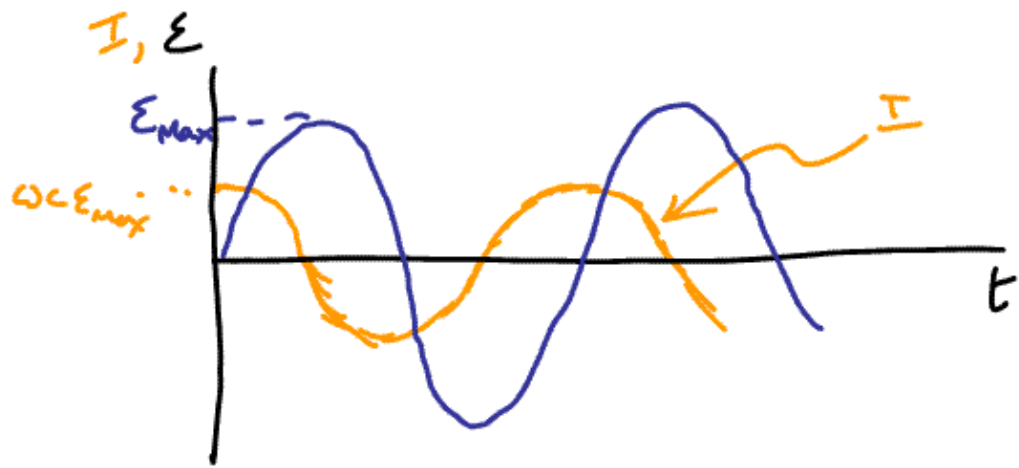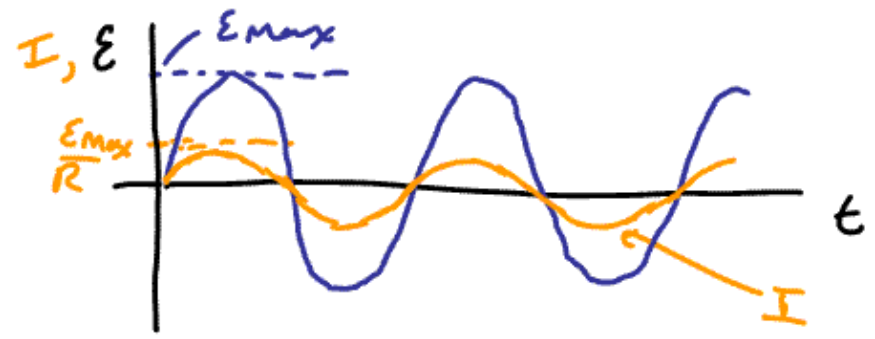

Graph to illustrate
relative phases and signs
of EMF terms

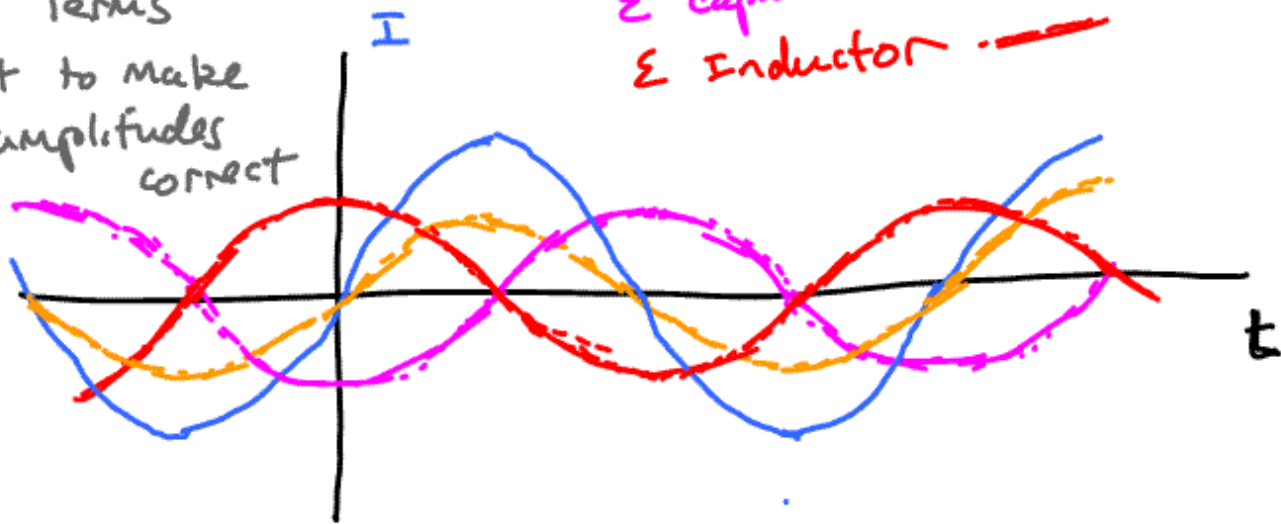No attempt to make
relative amplitudes
correct



\mathcal{E} Resistor ———
 \mathcal{E} capacitor - - - -
 \mathcal{E} Inductor - - - -

10

$$\mathcal{E} = \underbrace{\Delta V_R}_{R I_{\max} \sin(\omega t + \phi)} + \underbrace{\Delta V_C}_{-X_C I_{\max} \cos(\omega t + \phi)} + \underbrace{\Delta V_L}_{X_L I_{\max} \cos(\omega t + \phi)}$$

$$R I_{\max} \sin(\omega t + \phi)$$

$$-X_C I_{\max} \cos(\omega t + \phi)$$

$$X_L I_{\max} \cos(\omega t + \phi)$$

often people use a graphical analysis
with I and \mathcal{E} vectors rotating
in a plane \rightarrow phasors [see Ohanian p. 1047]

I think earlier edition of Ohanian did a nice treatment
using Math + Trig ID's \rightarrow get

$$\tan \phi = \frac{\chi_L - \chi_C}{R}$$

11

$$I_{\text{Max}} = \frac{\epsilon_{\text{Max}}}{\sqrt{R^2 + (\chi_L + \chi_C)^2}}$$

plays Role of
"R" in
LRC
circuit

≡ Impedance ≡ Z


$$\textcircled{A} \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

have ω at freq ω

$$\text{look at } \omega \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z \rightarrow \sqrt{R^2 + \left(\frac{L}{\sqrt{LC}} - \frac{\sqrt{LC}}{C}\right)^2} \textcircled{B}$$



→ maximizes I

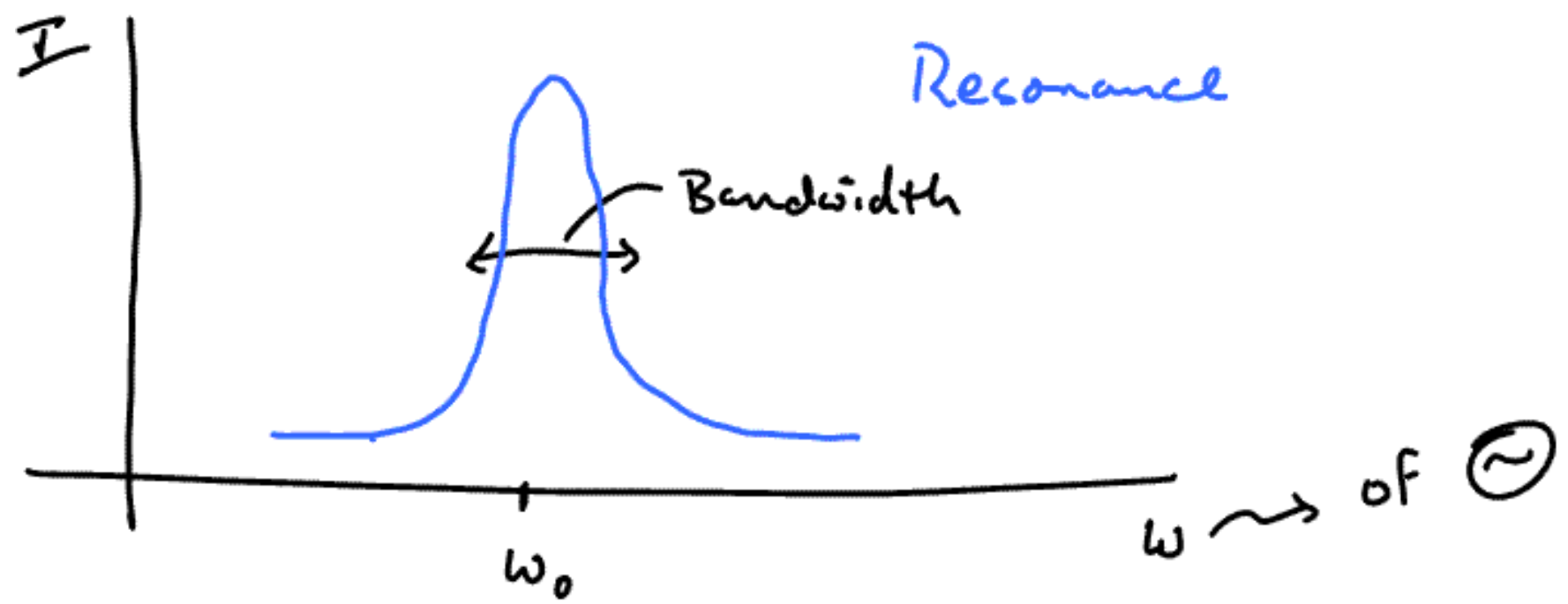

can imagine how useful this might be
Radio tuner for example ...

Magnetic fields in matter

13

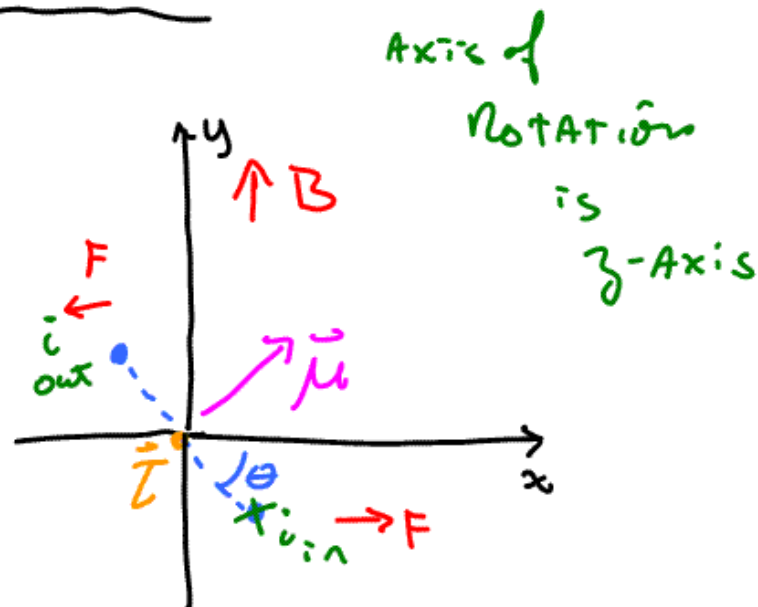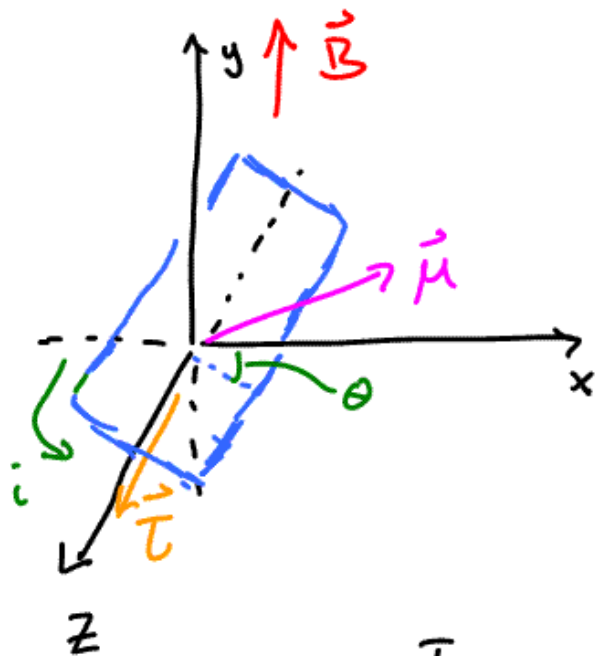

Torque on current loop = $\vec{\mu} \times \vec{B} = \vec{\tau}$
Dipole



Dipole magnetic field

Define Magnetic Moment of current loop $\equiv I A = |\vec{\mu}|$

← cross sect. Area of loop

Paramagnetic



Diamagnetic



No dipole

Ferromagnetic



Will come back to this
...