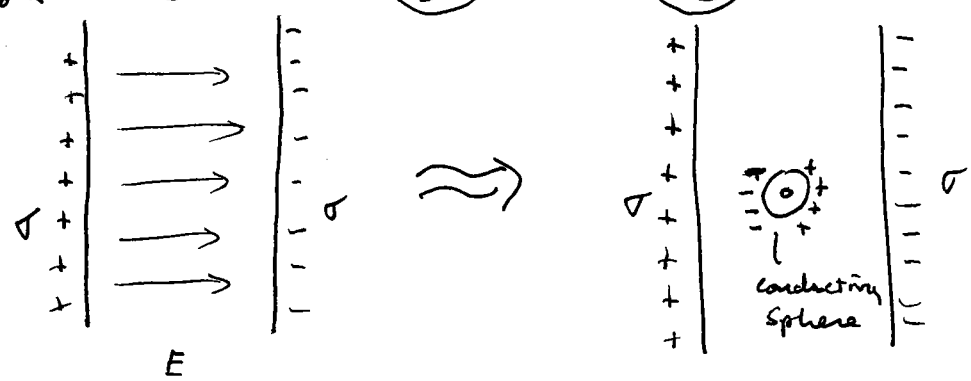



500 SHEETS FILLER 5 SQUARE
 50 SHEETS EYE-EASY 5 SQUARE
 100 SHEETS EYE-EASY 5 SQUARE
 42-382 100 SHEETS EYE-EASY 5 SQUARE
 42-382 100 RECYCLED WHITE 5 SQUARE
 42-389 200 RECYCLED WHITE 5 SQUARE
 Made in U.S.A.

Dielectrics - insulator - charges do not flow freely
 can become polarized

Polar vs. nonpolar




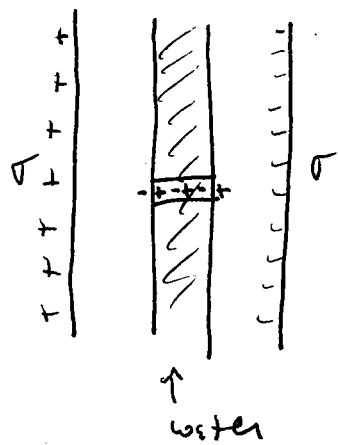Force between plates (E field)
 increased due to induced charges



dipoles line up ... get induced surface charge
 Again E at plates increased slightly
 (Less than if had placed conductor)

But inside dielectric

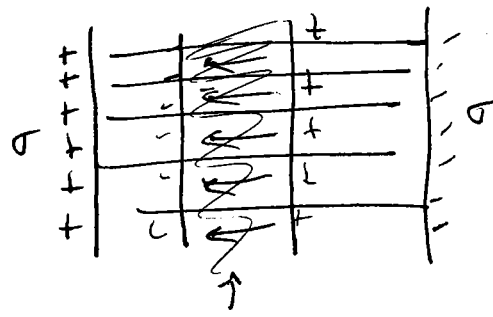

E is reduced

So, can reduce E between plates by filling w/ dielectric

So $|E| = \frac{V}{K \epsilon_0}$

reduced by $K \equiv$ dielectric constant $\epsilon > 1$


Water $K = 80.4$

Air $K = 1.00054$

Vacuum $K \approx 1$

Oil $K = 4.5$

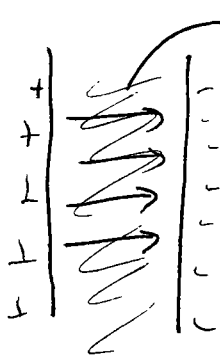Fields are affected by medium
effect is medium-dependent



$$E = \frac{J}{\kappa \epsilon_0}$$

$$dV = -\vec{E} \cdot d\vec{s}$$

$$|\Delta V| = V_{\text{between plates}} = \frac{J}{\kappa \epsilon_0} d = \frac{Q}{A} \frac{d}{\kappa \epsilon_0}$$

Earlier, w/ no dielectric

$$Q = CV \quad C \text{ was } \frac{\epsilon_0 A}{d}$$


Now

$$C = \frac{\kappa \epsilon_0 A}{d}$$

capacitance is increased!

~~Also~~

for a pt charge imbedded in dielectric

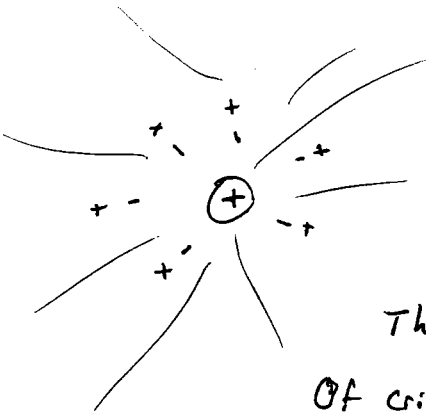

$$E \rightarrow \frac{1}{4\pi \kappa \epsilon_0} \frac{Q}{r^2}$$

$\epsilon_0 \rightarrow \kappa \epsilon_0$

This is all I will say.


Of critical importance to biology + chemistry

This is something you must deal w/ in real world
real solutions, real gusses, real cells, real expts.

This is the source of all sorts of optical effects!

~~Remember to read over the MCATS... do work to spend
more lecture time on it.~~

Current and Circuits

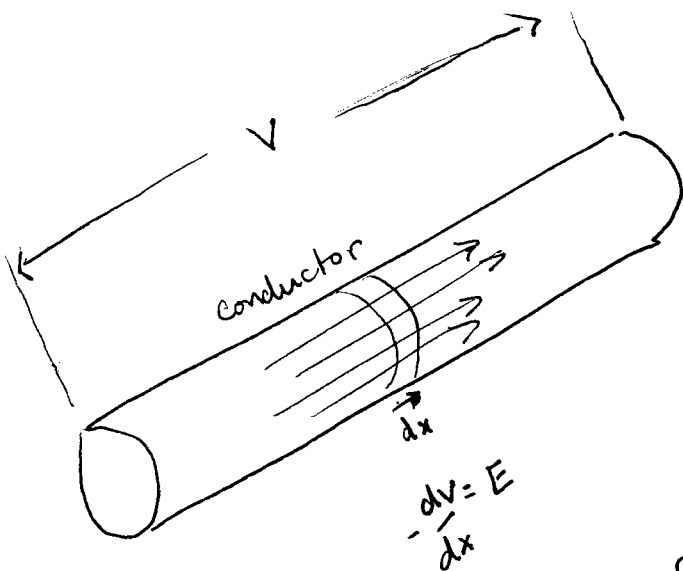

use v in place of ΔV \equiv conventional way to simplify notation

length L

E for uniform wire

$$E = \frac{V}{L}$$


$$-\frac{dV}{dx} = E$$

Charge flows

(Actually electrons)

but convention is \leftarrow

Direction of '+' charge flow is +

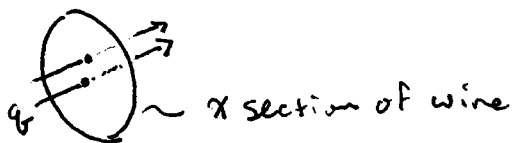


$$\frac{dq}{dt} \equiv \text{Current } i$$

i is (+) in direction of + charge flow

~~If no other source~~

If little conductor section is isolated Then charge flows until field due to induced charges cancels initial imposed field

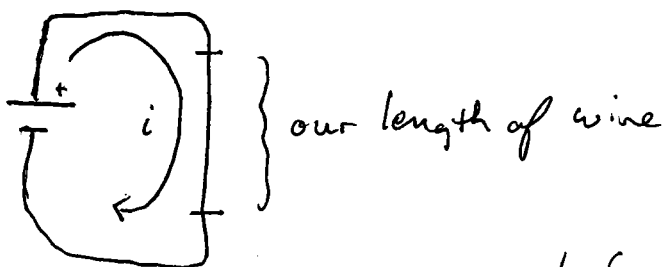
If not isolated but part of a circuit — charge goes around and around




Current units : 1 Ampere = $\frac{1 \text{ Coulomb}}{1 \text{ Second}}$

134784 50 SHEETS, FILLER, 3 SOLVANE
42-291 50 SHEETS, EYE-CASE, 3 SOLVANE
42-292 200 SHEETS, EYE-CASE, 3 SOLVANE
42-293 200 SHEETS, EYE-CASE, 3 SOLVANE
42-294 100 RECYCLED WHITE, 3 SOLVANE
42-295 200 RECYCLED WHITE, 3 SOLVANE
Made in U.S.A.

National Brand

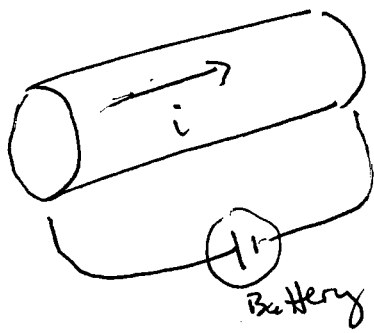

charge is not continuously accelerated

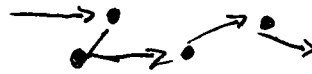


~~get a steady state equilibrium between i induced by E and lattice atoms~~

little collisions w/ atoms in the conductor lattice
Transfer energy from i moving charges to the lattice
(vibration + heat)

For given material get certain i for given V

for ohmic materials $i \propto V$ or $V = iR$
Resistance

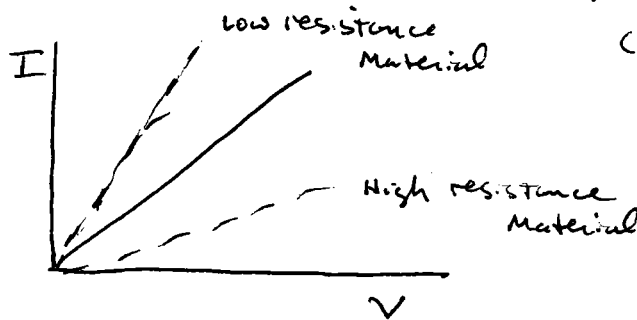
$$1 \Omega \equiv 1 \frac{\text{Volt}}{\text{Ampere}} \text{ (ohm)}$$




All materials have resistance except something called a "superconductor"

Except when explicitly said in problem - assume metal conductors - wires to have no/low resistance

Circuit Diagram

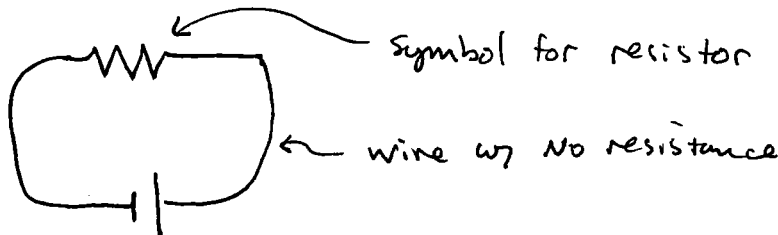


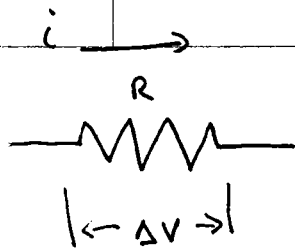

$$\Delta V = V = iR$$

V is said to be the "potential drop across the resistor"

useful analogy for circuits

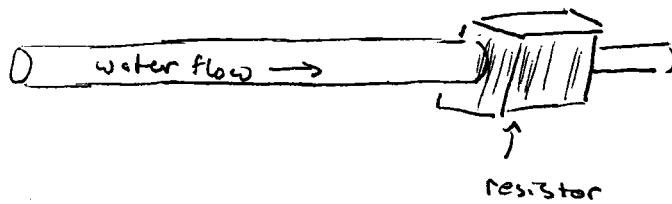

pipe width \downarrow



or



slats to slow flow

$$\frac{W}{q} = V \text{ across resistor}$$

$$W = qV$$

$$\frac{dW}{dt} = \frac{dq}{dt} V \Rightarrow P = iV$$

Power = (Current) (Voltage)

dissipated
in resistor

across resistor


also $V = iR$

$$P = i^2 R$$

13-782
 42-382
 42-382
 42-389
 42-382
 42-382
 42-389
 42-389
 500 SHEETS, FILLER, 8 SQUARE
 100 SHEETS, FILLER, 8 SQUARE
 100 SHEETS, FILLER, 8 SQUARE
 200 SHEETS, FILLER, 8 SQUARE
 100 SHEETS, FILLER, 8 SQUARE
 100 RECYCLED WHITE 8 SQUARE
 200 RECYCLED WHITE 8 SQUARE
 Made in U.S.A.


National Brand

Combinations of Resistors

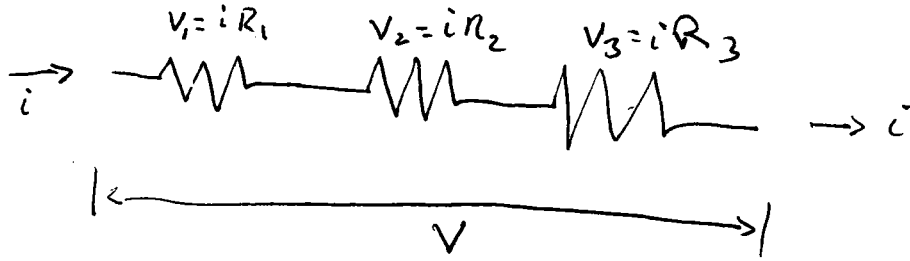

$$V = V_1 + V_2 + V_3 = i(R_1 + R_2 + R_3)$$

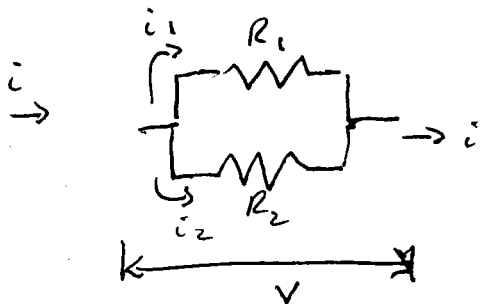Resistors in series: $R = R_1 + R_2 + R_3$



$$i = i_1 + i_2$$

$$V = iR$$

$$V = V_1 = i_1 R_1$$

$$V = V_2 = i_2 R_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Resistors in Parallel

Batteries and EMF

Batteries + Generators: able to maintain

≡ Seats of electromotive force

